

California Institute of Technology  
Department of Computer Science  
Computer Architecture

CS184a, Fall 2000

Background Questionnaire

Monday, September 25

---

Please answer the following questions and return before leaving class today. This will **not** be used to affect your grade or enrollment in this class. I will use it to understand what students already know and how much variance there is among your backgrounds so I can better plan the course.

1. Name:
2. Email address:
3. Your status, year, and option (*e.g.* G1 CS):
4. What related courses have you taken? (if you've taken a non-caltech equivalent, please list what and where)
  - EE4 (digital logic)
  - EE5x (microprocessor/logic project lab)
  - CS20 (intro computer science)
  - CS181 (VLSI)
  - CS237 (compiler)
5. Other courses you are taking this semester (best estimate, fine):
6. Reduce the following to Minimum Sum-of-Products form:
  - $\bar{a} \cdot \bar{b} \cdot c + \bar{a} \cdot b \cdot \bar{c} + a \cdot b \cdot \bar{c} + a \cdot \bar{b} \cdot c$
  - $(a + b) \cdot (b + \bar{c})$
  - $(a + b) \cdot (\bar{b} + \bar{c})$
  - $\overline{(b + c)} \cdot \overline{(a \cdot b)}$
7. How does the area of addition scale with  $n$ , the number of inputs to each of the operands? (delay?)


8. How does the area of an **arbitrary**  $n$ -input function scale with  $n$ ? (delay? – explain your assumptions)

9. Express the following in Two's complement (8b words):


	← MSB							
decimal 10								
0								
decimal -1								
hexadecimal 23								
decimal -2								

10. Draw an ADDER bit-slice using only two-input NAND gates.

 11. Write or draw logic to implement the following finite-state machine (one transition per clock,  $in$  is input,  $o0$ ,  $o1$  outputs):



 12. What is the function of this circuit?



13. Identify the Latency and Throughput of above circuit (each gate = 1 time unit):
  
14. Describe a function which cannot be implemented in purely digital logic:
  
15. Briefly describe the relative benefits of each of the following (*i.e.* why/when would I want to use each over the alternatives?)
  - microprocessor
  - custom logic (ASIC)
  - PAL or FPGA