

# CS184a: Computer Architecture (Structures and Organization)

Day10: October 25, 2000

Computing Elements 2:  
Cascades, ALUs, PLAs

## Last Time

- LUTs
  - area
  - structure
  - big LUTs vs. small LUTs with interconnect
  - design space
  - optimization

# Today

- LUT Delay
- LUT Cascades
- ALUs
- PLAs


# Delay

# Delay?

- Circuit Depth in LUTs?
- “Simple Function” --> M-input AND
  - 1 table lookup in M-LUT
  - $\log_k(M)$  in K-LUT
 
# Delay?


- M-input “Complex” function
  - 1 table lookup for M-LUT
  - between:  $\lceil (M-K)/\log_2(k) \rceil + 1$
  - and  $\lceil (M-K)/\log_2(k - \log_2(k)) \rceil + 1$



# Delay


- Simple:  $\log M$
- Complex: linear in  $M$
- Both go as  $1/\log(k)$

# Circuit Depth vs. K

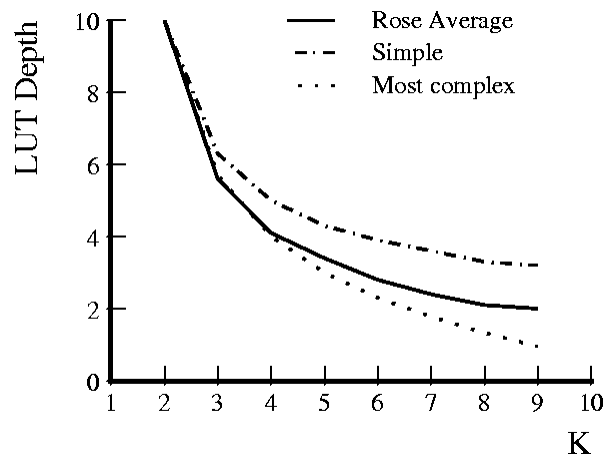

 
# LUT Delay vs. K

- For small LUTs:
  - $t_{LUT} \approx c_0 + c_1 \times K$
- Large LUTs:
  - add length term
  - $c_2 \times \sqrt{2^K}$
- Plus Wire Delay
  - $\sim \sqrt{\text{area}}$



# Delay vs. K

 

Why not satisfied with this model?

$$\text{Delay} = \text{Depth} \times (t_{LUT} + t_{\text{Interconnect}})$$

## Observation


- General interconnect is expensive
- “Larger” logic blocks
  - => less interconnect crossing
  - => lower interconnect delay
  - => get larger
  - => get slower
    - faster than modeled here due to area
  - => less area efficient
    - don't match structure in computation

## Different Structure

- How can we have “larger” compute nodes (less general interconnect) without paying huge area penalty of large LUTs?
 
# Structure in subgraphs

- Small LUTs capture structure
- Structure of small LUT-mapped netlists?





Caltech CS184a Fall2000 -- DeHon

13


# Structure

- LUT sequences ubiquitous

  


Caltech CS184a Fall2000 -- DeHon

# Hardwired Logic Blocks

 


Single Output

Caltech CS184a Fall2000 -- DeHon

 


15

# Hardwired Logic Blocks

 

Two outputs

Caltech CS184a Fall2000 -- DeHon

 

16




## Relation to ALUs

- How do ALUs differ?

## PLAs


# PLA

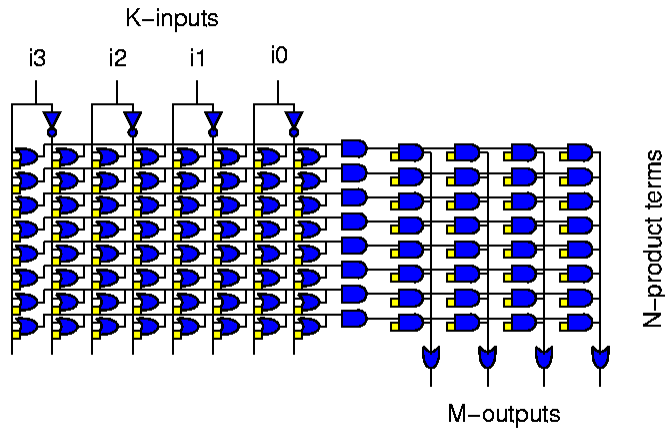

Caltech CS184a Fall2000 -- DeHon

19


# PLA and Memory

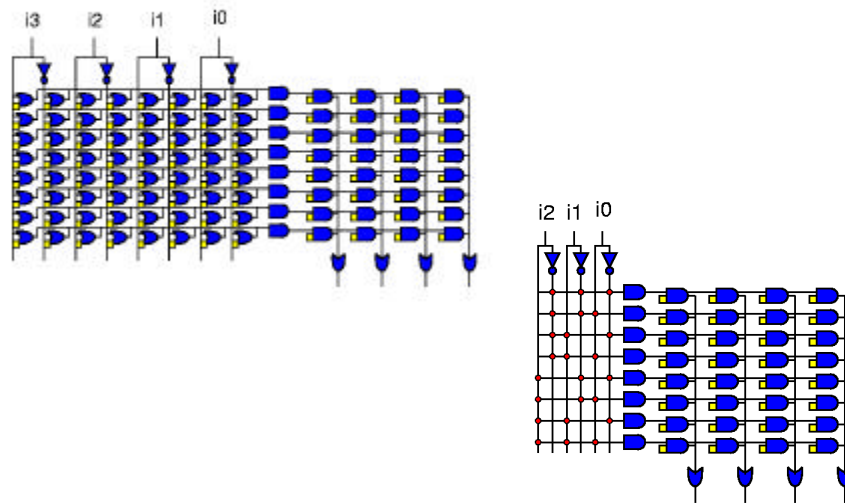

Caltech CS184a Fall2000 -- DeHon

)

## PLA and PAL

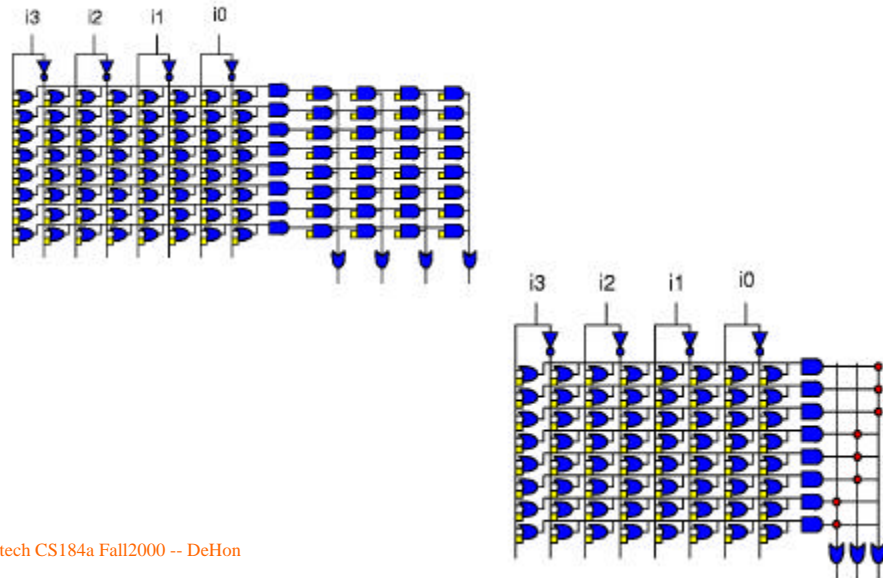

## PLAs

- Fast Implementations for large ANDs or Ors
- Number of P-terms can be exponential in number of input bits
  - most complicated functions
- Can use arrays of small PLAs
  - to exploit structure
  - like we saw arrays of small memories last time


## PLAs vs. LUTs?

- Look at Inputs, Outputs, P-Terms
  - minimum area (one study, see paper)
  - $K=10, N=12, M=3$
- A(PLA 10,12,3) comparable to 4-LUT?
  - 80-130%?
  - 300% on ECC (structure LUT can exploit)
- Delay?
  - Claim 40% fewer logic levels
    - (general interconnect crossings)

Caltech CS184a Fall2000 -- DeHon

23


## PLA Optimization (Folding)

 

Caltech CS184a Fall:

24

# Conventional/Commercial FPGA

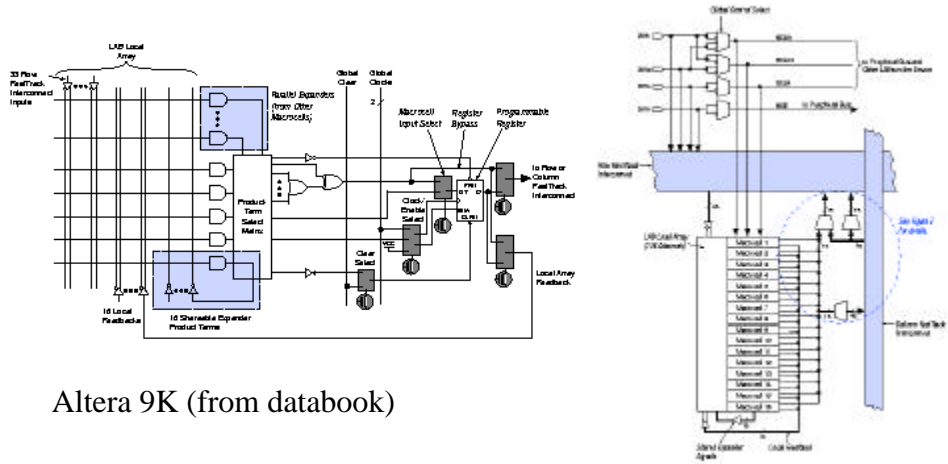


Altera 9K (from databook)

Caltech CS184a Fall2000 -- DeHon

25

# Conventional/Commercial FPGA

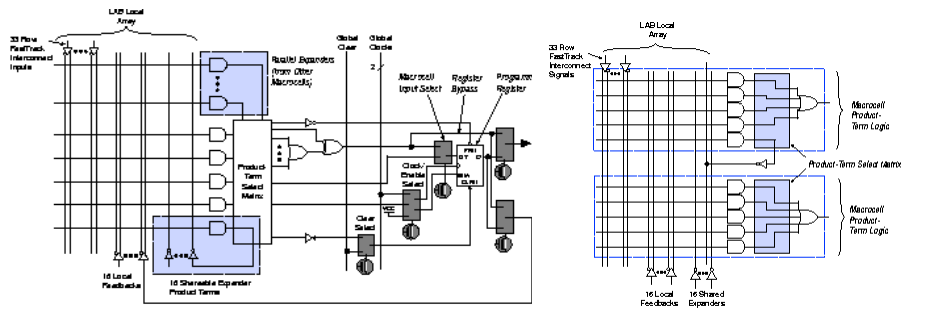

Altera 9K (from databook)

Caltech CS184a Fall2000 -- DeHon

26

## Finishing Up...

## Admin

- Homework 2 return
- Questions about homework

## Big Ideas [MSB Ideas]

- Programmable Interconnect allows us to exploit that structure
  - want to match to application structure
- Hardwired Cascades
  - key technique to reducing delay in programmables
- PLAs
  - canonical two level structure
  - hardwire portions to get Memories, PALs

Caltech CS184a Fall2000 -- DeHon

29

## Big Ideas [MSB-1 Ideas]

- Delay
  - LUT depth decreases with  $K$ 
    - in practice closer to  $\log(K)$
  - Delay increases with  $K$ 
    - small  $K$  linear + large fixed term
    - minimum around 5-6
- Better structure match with hardwired LUT cascades

Caltech CS184a Fall2000 -- DeHon

30