

California Institute of Technology  
Department of Computer Science  
Computer Architecture

CS184a, Winter 2003

Assignment 1: Logic

Monday, January 6

**Due:** Monday, January 13, 9:00AM

You may do sections (A and B) or (B and C). C is primarily intended as a more challenging (interesting) alternative for students who have already had considerable experience with digital logic.

You may use hierarchical schematics. Where appropriate quantities are 4b, unsigned numbers. Use of a schematic drawing program for circuits is encouraged.

## A: Basic Logic

1. Implement  $A > B$  out of 2-input NAND gates.
2. Show the logic (in basic gates and registers) for a simple vending machine.
  - Inputs: n, d, and q, (nickle, dime, quarter)
  - Output: v (vend), nc (nickle change)
  - Function: Collect  $\geq 30$  cents, then vend and give change in nickles.Don't worry about running nout of nickles to provide as change.  
Include a diagram of your state-transition graph in your writeup.
3. Using your comparison function from A.1, show logic for a spatial sorting function to sort 4, 4b inputs into ascending order.

## B: Properties of Boolean Functions

1. Consider all two-input functions. For each identify if universal; you may tie the inputs of a function to a constant 0 or 1.
2. Counting each gate as unit size, give a bound on the size difference between an optimal implementation of an arbitrary  $n$ -input function when the implementation may use an optimal mixture of the full set of 2-input functions from B.2 as gates compared to an implementation which uses only 2-input nand gates.

## C: Advanced Logic Problems

1. Consider  $n$ -input functions. Using only two-input NAND gates, give a bound on the number of functions that can be implemented with depth  $l$ . Compare your result to B.1. (Your bound should be non-trivial, but does not need to be tight.)
2. How does your answer to C.1 change if you can use any 2-input function? 3-input function?
3. Firing Squad – Design the logic for an FSmodule.
  - FSmodules can be assembled into a 1d array of arbitrary length.
  - Each FSmodule is connected exclusively to his left and right neighbors.
  - The leftmost FSmodule will get a start input.
  - FSmodules may have configuration input bits which distinguish the leftmost and rightmost modules from the rest (*i.e.* a module will be leftmost, rightmost, or a chained element).
  - All FSmodules are clocked together.
  - Data can travel from one FSmodule to his adjacent neighbor in one cycle.
  - You can have a constant number of wires between adjacent FSmodules (independent of the length of the 1d array).
  - The state in an FSmodule is finite and independent of the length of the 1d array.
  - In response to an input pulse on the leftmost module, the array of FSmodules should all, simultaneously flash an output light.
  - The number of cycles between the input pulse and the synchronized firing of the FSmodules' lights is not restricted.

Show your state-transition graph and gate logic. Describe the operation of your solution.