

CS184a: Computer Architecture (Structure and Organization)

Day 10: January 31, 2003
Compute 2:



Caltech CS184 Winter2003 -- DeHon

Last Time

- LUTs
 - area
 - structure
 - big LUTs vs. small LUTs with interconnect
 - design space
 - optimization

Caltech CS184 Winter2003 -- DeHon

Today

- Cascades
- ALUs
- PLAs

Last Time


- Larger LUTs
 - Less interconnect delay
- General: Larger compute blocks
 - Minimize interconnect
- Large LUTs
 - Not efficient for typical logic structure

Different Structure

- How can we have “larger” compute nodes (less general interconnect) without paying huge area penalty of large LUTs?



Structure in subgraphs

 - Small LUTs capture structure
- What structure does a small-LUT-mapped netlist have?





Structure

- LUT sequences ubiquitous

  

Caltech CS184 Winter2003 -- DeHon


Hardwired Logic Blocks

  

Single Output


Caltech CS184 Winter2003 -- DeHon

Hardwired Logic Blocks

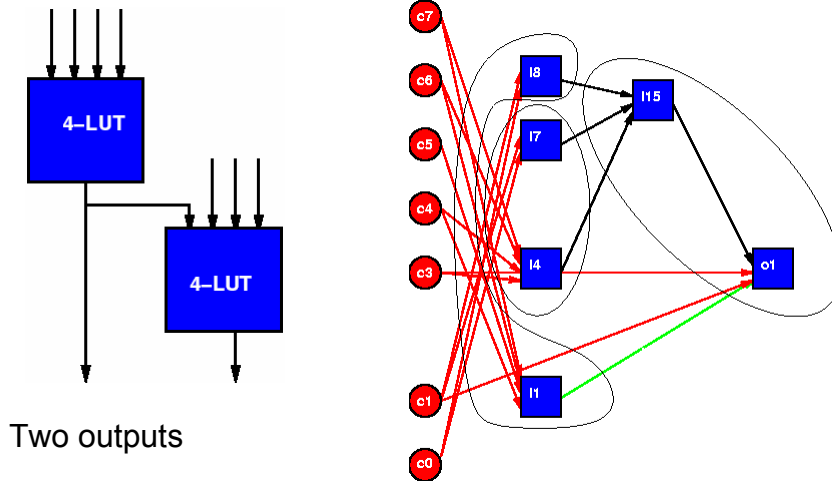


Two outputs

Delay Model

 

- $T_{\text{cascade}} = T(3\text{LUT}) + T(\text{mux})$

Options

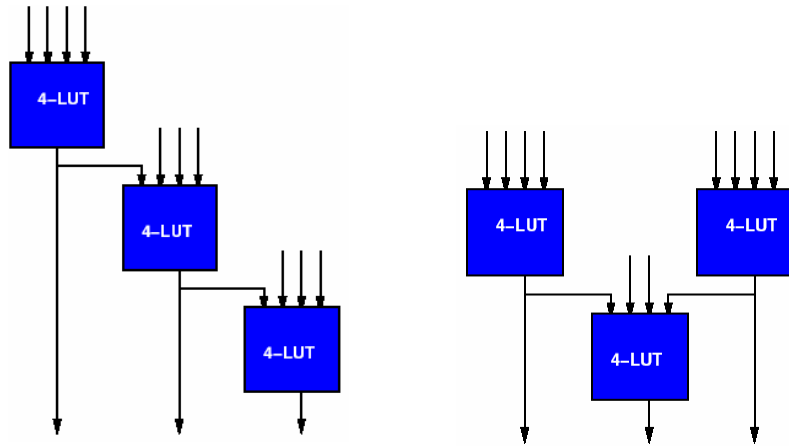

Chung & Rose Study

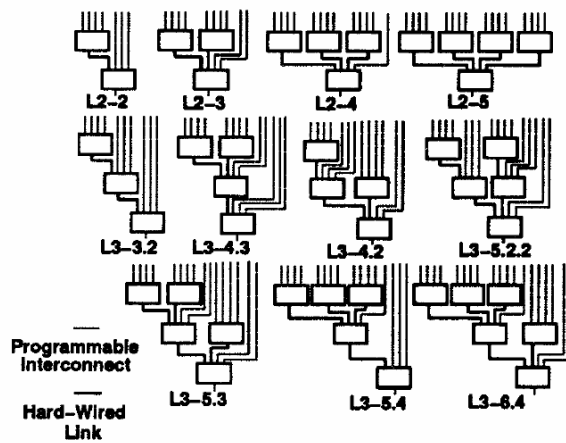


Figure 8: Delay Study HLB Topologies

Cascade LUT Mappings

Logic Block	$\overline{N_R}$	% decr in $\overline{N_R}$	$\overline{D_{tot}}$ (ns)	% decr in $\overline{D_{tot}}$
K4	5.4	0	30	0
L2-2	4.2	22	26	13
L2-3	3.4	37	22	27
L2-4	3.1	43	21	30
L2-5	3.0	44	21	30
L3-3.2	4.0	26	25	17
L3-4.2	3.0	44	21	30
L3-4.3	3.1	43	21	30
L3-5.2.2	3.1	43	21	30
L3-5.3	3.0	44	21	30
L3-5.4	2.9	46	20	33
L3-6.4	2.8	48	20	33


Table 3: Delay Performance of Different HLBs

[Chung & Rose, DAC '92]


Bench Cct	3-inp L2-3	X4000 CLB	4-inp L2-3	4-inp L3-4.2
9symml	40	36	26	19
alu2	77	71	48	37
alu4	126	122	82	61
apex7	44	38	27	20
b9	22	20	16	12
c1355	131	91	80	59
c8	21	17	15	11
cc	17	8	9	7
cm162a	8	5	5	4
comp	27	17	14	13
count	21	21	14	10
decod	10	10	8	8
mux	10	5	5	5
vda	96	97	70	52
z4ml	3	3	3	2
Tot HLBs	653	561	421	320
LUT Bits	15672	22440	20208	20480
Ratios	0.70	1	0.90	0.91
HLB pins	6530	6171	5473	5440
Ratios	1.06	1	0.89	0.88

Table 2: Area Measures of Different HLBs

ALU vs. Cascaded LUT?

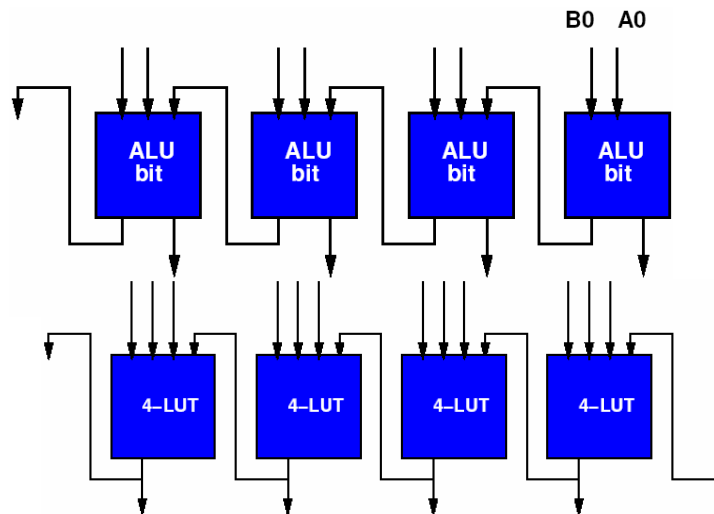

4-LUT Cascade ALU

 

Caltech CS184 Winter2003 -- DeHon

15

ALU vs. LUT ?


- Compare/contrast
- ALU
 - Only subset of ops available
 - Denser coding for those ops
 - Smaller
 - ...but interconnect dominates

Caltech CS184 Winter2003 -- DeHon

16

Parallel Prefix LUT Cascade?

 
- Can compute LUT cascade in $O(\log(N))$ time?
- Can compute mux cascade using parallel prefix?



- Can make mux cascade associative?


Parallel Prefix Mux cascade

 - How can mux transform $S \rightarrow \text{mux-out}$?
 - $A=0, B=0 \rightarrow \text{mux-out}=0$
 - $A=1, B=1 \rightarrow \text{mux-out}=1$
 - $A=0, B=1 \rightarrow \text{mux-out}=S$
 - $A=1, B=0 \rightarrow \text{mux-out}=\neg S$




Parallel Prefix Mux cascade

 - How can mux transform $S \rightarrow \text{mux-out}$?
 - $A=0, B=0 \rightarrow \text{mux-out}=0$ Stop= S
 - $A=1, B=1 \rightarrow \text{mux-out}=1$ Generate= G
 - $A=0, B=1 \rightarrow \text{mux-out}=S$ Buffer = B
 - $A=1, B=0 \rightarrow \text{mux-out}=\neg S$ Invert = I



Parallel Prefix Mux cascade

 - How can 2 muxes transform input?
- Can I compute transform from 1 mux transforms?




Two-mux transforms

- $SS \rightarrow S$
- $GS \rightarrow S$
- $BS \rightarrow S$
- $IS \rightarrow S$
- $SG \rightarrow G$
- $GG \rightarrow G$
- $BG \rightarrow G$
- $IG \rightarrow G$
- $SB \rightarrow S$
- $GB \rightarrow G$
- $BB \rightarrow B$
- $IB \rightarrow I$
- $SI \rightarrow G$
- $GI \rightarrow S$
- $BI \rightarrow I$
- $II \rightarrow B$

Generalizing mux-cascade


- How can N muxes transform the input?
- Is mux transform composition associative?

Parallel Prefix Mux-cascade

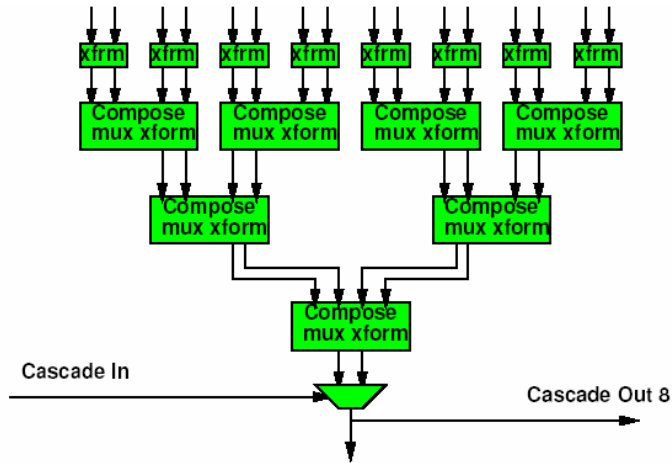


Commercial Devices

Xilinx XC4000 CLB

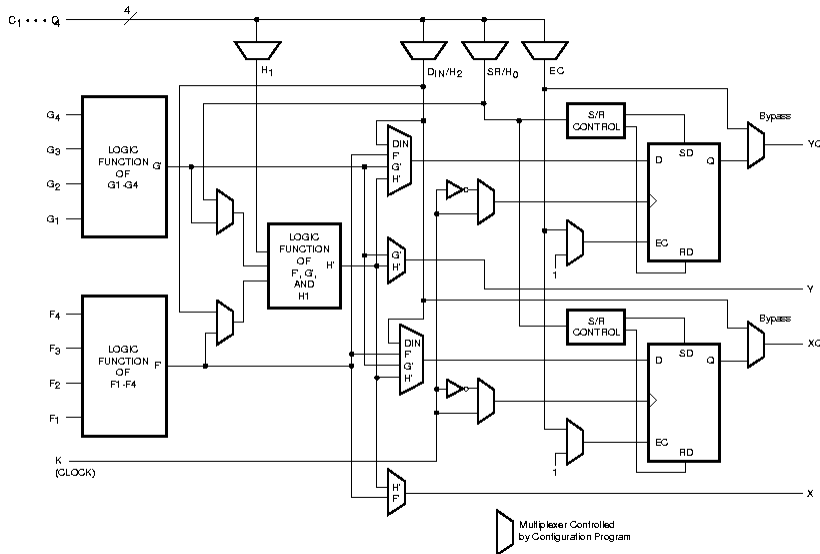

Caltech CS184 Winter2003 -- DeHon



Xilinx Virtex-II

 

DS031_32_101600

Figure 14: Virtex-II CLB Element

Caltech CS184 Winter2003 -- DeHon

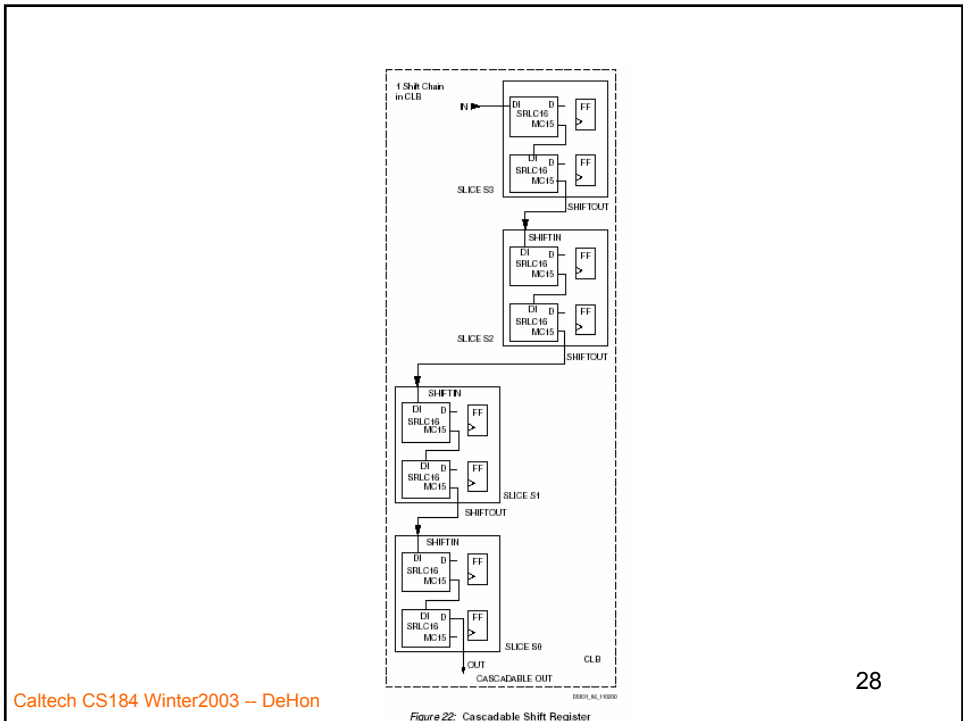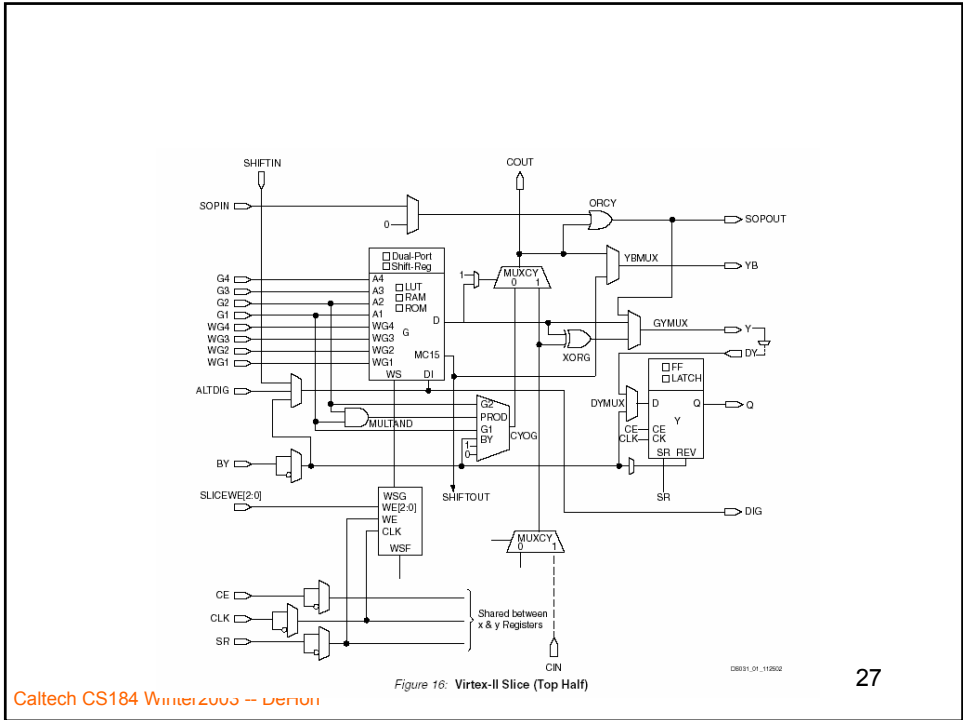

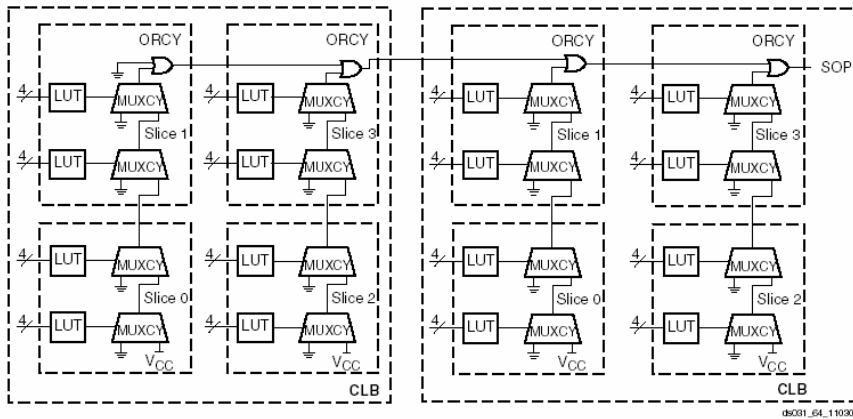


Figure 25: Horizontal Cascade Chain

Altera Stratix

Figure 5. Stratix LE

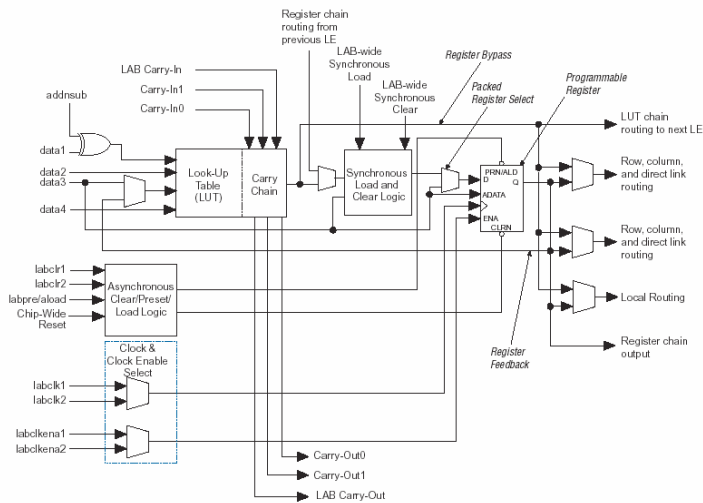


Figure 7. LE in Dynamic Arithmetic Mode


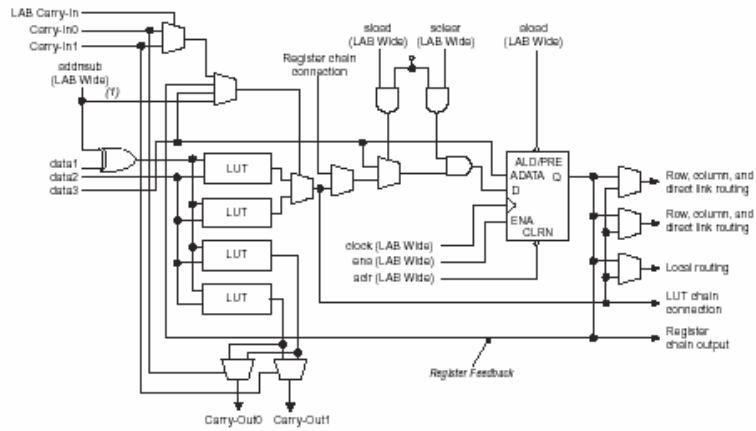


Figure 8. Carry Select Chain

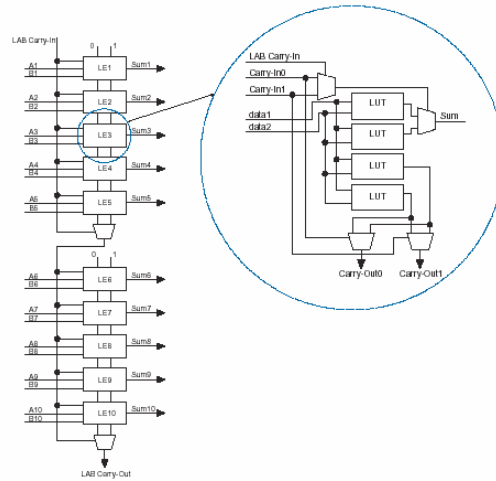


Programmable Array Logic (PLAs)

PLA

- Directly implement flat (two-level) logic
 - $O = a*b*c*d + !a*b!*d + b!*c*d$
- Exploit substrate properties allow wired-OR


Wired-or

 - Connect series of inputs to wire
- Any of the inputs can drive the wire high



Wired-or


- Implementation with Transistors

 

Programmable Wired-or

- Use some memory function to programmable connect (disconnect) wires to OR


- Fuse:

 

Caltech CS184 Winter2003 -- DeHon


Programmable Wired-or

- Gate-memory model

 


Caltech CS184 Winter2003

Diagram Wired-or

 


Wired-or array

 - Build into array
 - Compute many different **or** functions from set of inputs



Combined **or**-arrays to PLA

 
- Combine two **or** (**nor**) arrays to produce PLA (**and-or** array)



Caltech CS184 Winter2003 -- DeHon

PLA

 
- Can implement each **and** on single line in first array
- Can implement each **or** on single line in second array



Caltech CS184 Winter2003 -- DeHon

PLA

 - Efficiency questions:
 - Each **and/or** is linear in total number of potential inputs (not actual)
 - How many product terms between arrays?



Caltech CS184 Winter2003 -- DeHon

PLAs

- Fast Implementations for large ANDs or Ors
- Number of P-terms **can be** exponential in number of input bits
 - most complicated functions
 - not exponential for many functions
- Can use arrays of small PLAs
 - to exploit structure
 - like we saw arrays of small memories last time

Caltech CS184 Winter2003 -- DeHon


PLA Product Terms

- Can be exponential in number of inputs
- *E.g.* n-input **xor** (parity function)
 - When flatten to two-level logic, requires exponential product terms
 - $a*b+!a*b$
 - $a*!b*!c+!a*b*!c+!a*!b*c+a*b*c$
- ...and shows up in important functions
 - Like addition...


PLAs vs. LUTs?

- Look at Inputs, Outputs, P-Terms
 - minimum area (one study, see paper)
 - $K=10, N=12, M=3$
- $A(\text{PLA } 10, 12, 3)$ comparable to 4-LUT?
 - 80-130%?
 - 300% on ECC (structure LUT can exploit)
- Delay?
 - Claim 40% fewer logic levels (4-LUT)
 - (general interconnect crossings)



PLA

 

PLA and Memory

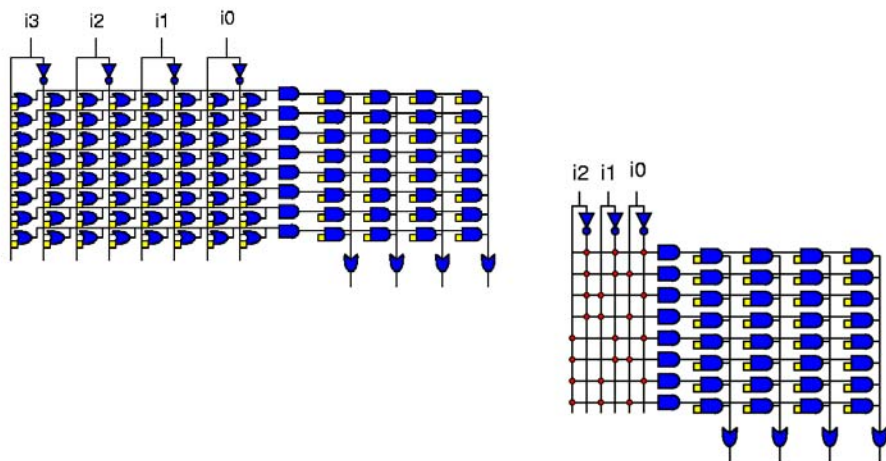



PLA and PAL

  

PAL = Programmable Array Logic

Caltech CS184 Winter2003 -- DeHon


Conventional/Commercial FPGA

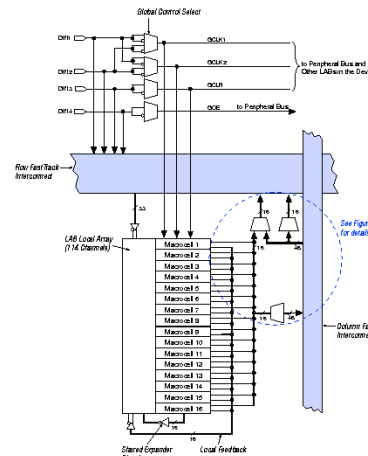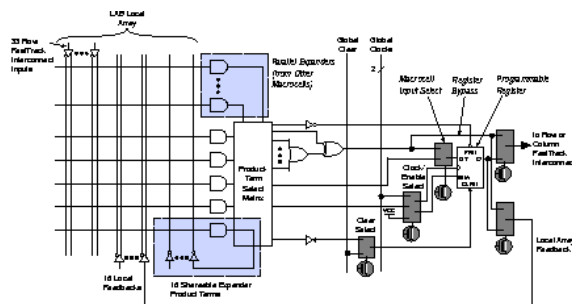

Altera 9K (from databook)

Caltech CS184 Winter2003 -- DeHon

Conventional/Commercial FPGA

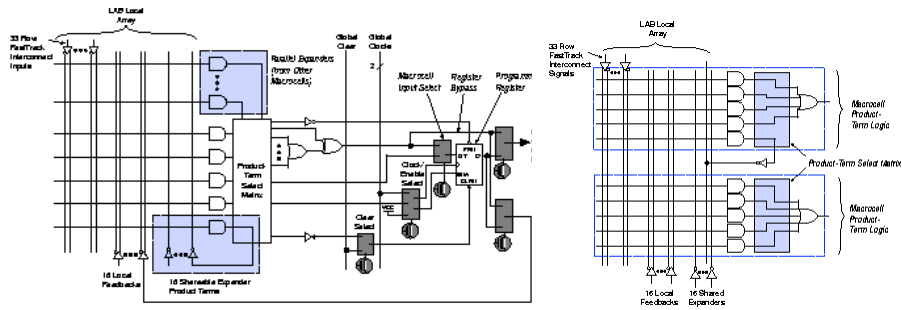

Altera 9K (from databook)

Big Ideas [MSB Ideas]

- Programmable Interconnect allows us to exploit that structure
 - want to match to application structure
 - Prog. interconnect delay expensive
- Hardwired Cascades
 - key technique to reducing delay in programmables
- PLAs
 - canonical two level structure
 - hardwire portions to get Memories, PALs

Big Ideas

[MSB-1 Ideas]

- Better structure match with hardwired LUT cascades