

CS184a: Computer Architecture (Structure and Organization)

Day 17: February 19, 2003
Retime 1: Transformations



Caltech CS184 Winter2003 -- DeHon

Previously

- Reviewed Pipelining
 - basic assignments on
- Saw spatial designs efficient
 - when reuse logic at maximum frequency
- Interconnect is dominant delay
 - and dominant area
 - heavy call to reuse to use efficiently


Caltech CS184 Winter2003 -- DeHon

Today

- Systematic transformation for retiming
 - preserve semantics (meaning)

Motivation

 - FPGAs (spatial computing)
 - run efficiently when all resources reused rapidly
 - cycle time minimized



- “Everything in the right place at the right time.”


Motivating Questions

- Can I build fixed-frequency (fixed clock) programmable architecture?
- Can I always make design run at maximum clock rate?
- How do we systematically transform any computation to
 - Operate on fixed-frequency array?
 - Coordinate around mandatory registers in design?

Task

- Move registers to:
 - Preserve semantics
 - Minimize path length between registers
 - *i.e.* Make path length 1 for maximum throughput or reuse
 - ...while minimizing number of registers required

Simple Example

 


Path Length (L) = 4


Can we do better?

Legal Register Moves


- Retiming Lag/Lead

 

Canonical Graph Representation

 


Observable I/O

 


Separate arc for each path
 Weight edges by number of registers
 (weight nodes by delay through node)

Critical Path Length

 

Observable I/O

 


Critical Path: Length of longest path of zero weight nodes

Compute in $O(|E|)$ time by levelizing network:

Topological sort, push path lengths forward until find register.

Retiming Lag/Lead

 

Retiming: Assign a lag to every vertex

$$\text{weight}(e') = \text{weight}(e) + \text{lag}(\text{head}(e)) - \text{lag}(\text{tail}(e))$$

Valid Retiming


- Retiming is valid as long as:
 - $\forall e$ in graph
 - $\text{weight}(e') = \text{weight}(e) + \text{lag}(\text{head}(e)) - \text{lag}(\text{tail}(e)) \geq 0$
- Assuming original circuit was a valid synchronous circuit, this guarantees:
 - non-negative register weights on all edges
 - no travel backward in time :-)
 - all cycles have strictly positive register counts
 - propagation delay on each vertex is non-negative (assumed 1 for today)

Retiming Task

- Move registers \equiv assign lags to nodes
 - lags define all locally legal moves
- Preserving non-negative edge weights
 - (previous slide)
 - guarantees collection of lags remains consistent globally

Retiming Transformation

 - *N.B.:* unchanged by retiming
 - number of registers around a cycle
 - delay along a cycle
- Cycle of length P must have
 - at least P/c registers on it
 - to be retimeable to cycle c



Optimal Retiming


- There is a retiming of
 - graph G
 - w/ clock cycle c
 - *iff* $G-1/c$ has no cycles with negative edge weights
- $G-\alpha \equiv$ subtract α from each edge weight

1/c Intuition

- Want to place a register every c delay units
- Each register adds one
- Each delay subtracts $1/c$
- As long as remains more positives than negatives around all cycles
 - can move registers to accommodate
 - Captures the $\text{regs} = P/c$ constraints

$G-1/c$

Observable I/O

 

Compute Retiming


- $\text{Lag}(v) = \text{shortest path to I/O in } G-1/c$
- Compute shortest paths in $O(|V||E|)$
 - Bellman-Ford
 - also use to detect negative weight cycles when c too small

Bellman Ford

- For $l \leftarrow 0$ to N
 - $u_i \leftarrow -\infty$ (except $u_i = 0$ for IO)
- For $k \leftarrow 0$ to N
 - for $e_{i,j} \in E$
 - $u_i \leftarrow \min(u_i, u_j + w(e_{i,j}))$
- For $e_{i,j} \in E$ *//still update \rightarrow negative cycle*
 - if $u_i > u_j + w(e_{i,j})$
 - cycles detected


Apply to Example

Observable I/O

 


Try $c=1$

Observable I/O

 


Observable I/O

 

Apply: Find Lags


Observable I/O

 

Negative weight cycles?
Shortest paths?


Apply: Lags

Observable I/O

 


Apply: Move Registers

Observable I/O

 


Observable I/O

 


$$\text{weight}(e') = \text{weight}(e) + \text{lag}(\text{head}(e)) - \text{lag}(\text{tail}(e))_{24}$$

Apply: Retimed

Observable I/O


 


Observable I/O

 


Apply: Retimed Design



Observable I/O

  



Revise Example (fanout delay)

 


Revised: Graph

  


Revised: Graph

  


Revised: C=1?

 


Revised: C=2?

 


Revised: Lag

 



Revised: Lag

 



Take ceiling to convert to integer lags:

 



Revised: Apply Lag

  

Revised: Apply Lag

  


Revised: Retimed

  



Pipelining

- We can use this retiming to pipeline
- Assume we have enough (infinite supply) registers at edge of circuit
- Retime them into circuit


$C > 1 \implies$ Pipeline

 

Add Registers

 
 


Pipeline Retiming: Lag

 


Pipelined Retimed



n=5

  

Real Cycle

 


Real Cycle

  


Caltec


Cycle $C=1$?

 


Cycle C=2?

 


Cycle: C-slow

 

 
Cycle=c \Rightarrow C-slow network has Cycle=1





2-slow Cycle $\Rightarrow C=1$

 



2-Slow Lags

 

2-Slow Retime

  

Retimed 2-Slow Cycle

  


C-Slow applicable?

- Available parallelism
 - solve C identical, independent problems
 - e.g. process packets (blocks) separately
 - e.g. independent regions in images
 - “Hyperthreading”
 - Is a fancy term for applying C-slow to processor execution
- Commutative operators
 - e.g. max example

Max Example


2-Slow design:

 

$X_2 X_2 X_1 X_1 X_0 X_0 \longrightarrow Y_2 ? Y_1 ? Y_0 ?$

$B_2 A_2 B_1 A_1 B_0 A_0 \longrightarrow YA_2 YB_1 YA_1 YB_0 YA_0 ?$

Max Example

 


**Computes two
interleaved streams:
even max, odd max**

**Computes final
max of even and
odd pairs**

HSRA Retiming

 
- HSRA
 - adds mandatory pipelining to interconnect
- One additional twist
 - long, pipelined interconnect
 - \Rightarrow need more than one register on paths



Accommodating HSRA Interconnect Delays

- Add buffers to LUT→LUT path to match interconnect register requirements
- Retime to $C=1$ as before
- Buffer chains force enough registers to cover interconnect delays

Accommodating HSRA Interconnect Delays

 

Big Ideas

[MSB Ideas]

- Retiming transformations important to
 - minimize cycles
 - efficiently utilize spatial architectures
- Optimally solvable in $O(|V||E|)$ time
- Tells us
 - pipelining required
 - C-slow
 - where to move registers
- Can accommodate mandatory delays