

# CS184a: Computer Architecture (Structure and Organization)

Day 3: January 13, 2003  
Arithmetic and Pipelining



Caltech CS184 Winter2003 -- DeHon

## Last Time

- Boolean logic  $\Rightarrow$  computing **any** finite function
- Sequential logic  $\Rightarrow$  computing **any** finite automata
  - included some functions of unbounded size
- Saw gates and registers
  - ...and a few properties of logic

Caltech CS184 Winter2003 -- DeHon

# Today

- Addition
  - organization
  - design space
  - area, time
- Pipelining
- Temporal Reuse
  - area-time tradeoffs

Caltech CS184 Winter2003 -- DeHon

## Example: Bit Level Addition

- Addition
  - (everyone knows how to do addition base 2, right?)

**C: 1101101000**

**A: 01101101010**

**B: 01100101100**

**S: 11110010110**

Caltech CS184 Winter2003 -- DeHon

## Addition Base 2

- $A = a_{n-1} * 2^{(n-1)} + a_{n-2} * 2^{(n-2)} + \dots + a_1 * 2^1 + a_0 * 2^0$   
 $= \sum (a_i * 2^i)$
- $S = A + B$
- $s_i = (\text{xor } \text{carry}_i \text{ (xor } a_i \text{ } b_i))$
- $\text{carry}_i = (a_{i-1} + b_{i-1} + \text{carry}_{i-1}) \geq 2$   
 $= (\text{or } (\text{and } a_{i-1} \text{ } b_{i-1}) \text{ (and } a_{i-1} \text{ } \text{carry}_{i-1})$   
 $\text{(and } b_{i-1} \text{ } \text{carry}_{i-1}))$

Caltech CS184 Winter2003 -- DeHon

## Adder Bit


- $S = (\text{xor } a \text{ } b \text{ } \text{carry})$
- $t = (\text{xor2 } a \text{ } b); s = (\text{xor2 } t \text{ } \text{carry})$
- $\text{xor2} = (\text{and } (\text{not } (\text{and2 } a \text{ } b))$   
 $\text{(not } (\text{and2 } (\text{not } a) \text{ (not } b))))$
- $\text{carry} = (\text{not } (\text{and2 } (\text{not } (\text{and2 } a \text{ } b))$   
 $(\text{and2 } (\text{not } (\text{and2 } b \text{ } \text{carry})) \text{ (not } (\text{and2 } a$   
 $\text{ } \text{carry}))))))$

Caltech CS184 Winter2003 -- DeHon

# Ripple Carry Addition


- Shown operation of each bit
- Often convenient to define logic for each bit, then assemble:

– bit slice

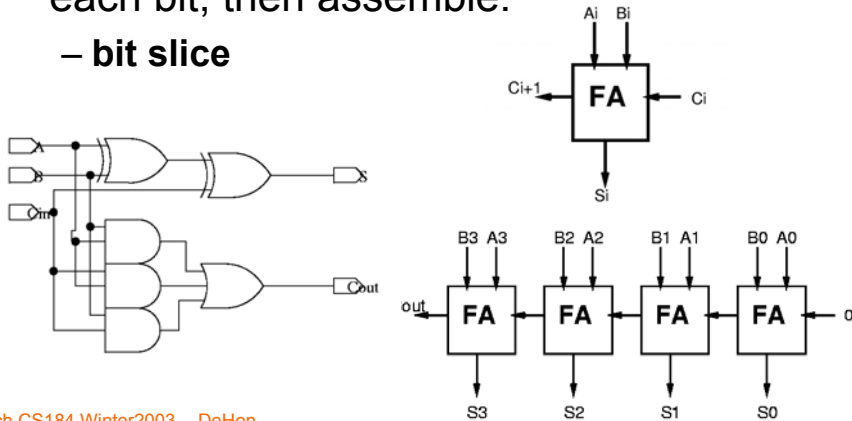

Caltech CS184 Winter2003 -- DeHon

# Ripple Carry Analysis

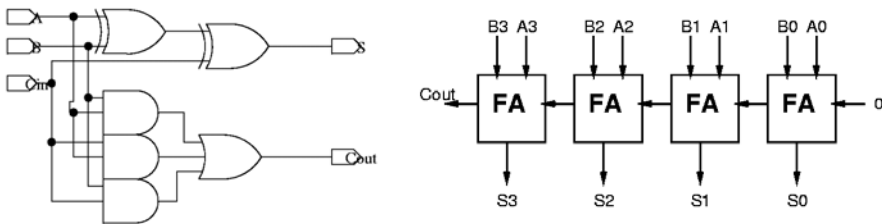

- Area:  $O(N)$  [ $6n$ ]
- Delay:  $O(N)$  [ $2n$ ]

Caltech CS184 Winter2003 -- DeHon

# Can we do better?

Caltech CS184 Winter2003 -- DeHon


## Important Observation

- Do we have to wait for the carry to show up to begin doing useful work?
  - We do have to know the carry to get the right answer.
  - But, it can only take on two values

Caltech CS184 Winter2003 -- DeHon
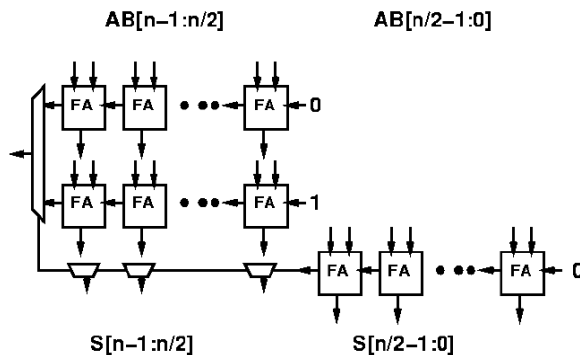
# Idea

- Compute both possible values and select correct result when we know the answer



Caltech CS184 Winter2003 -- D

# Preliminary Analysis

- DRA--Delay Ripple Adder
- $DRA(n) = k*n$
- $DRA(n) = 2*DRA(n/2)$
- DP2A-- Delay Predictive Adder
- $DP2A = DRA(n/2) + D(\text{mux}2)$
- ...almost half the delay!


Caltech CS184 Winter2003 -- DeHon

# Recurse

- If something works once, do it again.
- Use the predictive adder to implement the first half of the addition

Caltech CS184 Winter2003 -- DeHon

# Recurse

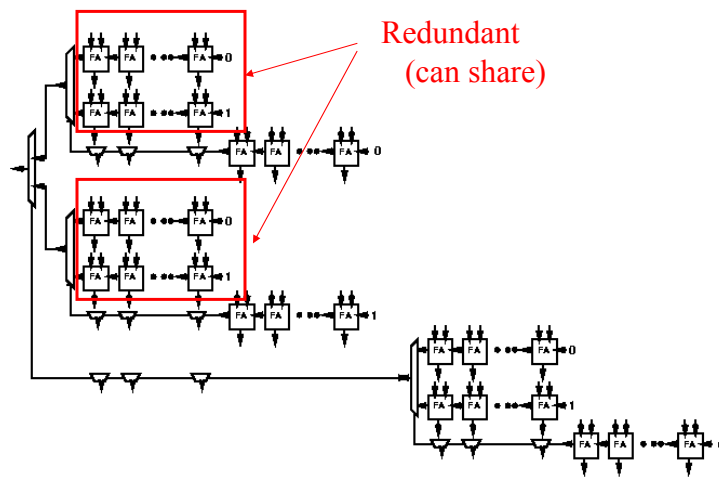

Caltech CS184 Winter2003 -- DeHon

## Recurse

- If something works once, do it again.
- Use the predictive adder to implement the first half of the addition
- $DP4A(n) = DRA(n/4) + D(\text{mux}2) + D(\text{mux}2)$
- $DP4A(n) = DRA(n/4) + 2 * D(\text{mux}2)$

Caltech CS184 Winter2003 -- DeHon


## Recurse

- By now we realize we've been using the wrong recursion
  - should be using the DPA in the recursion
- $DPA(n) = DPA(n/2) + D(\text{mux}2)$
- $DPA(n) = \log_2(n) * D(\text{mux}2) + C$

Caltech CS184 Winter2003 -- DeHon



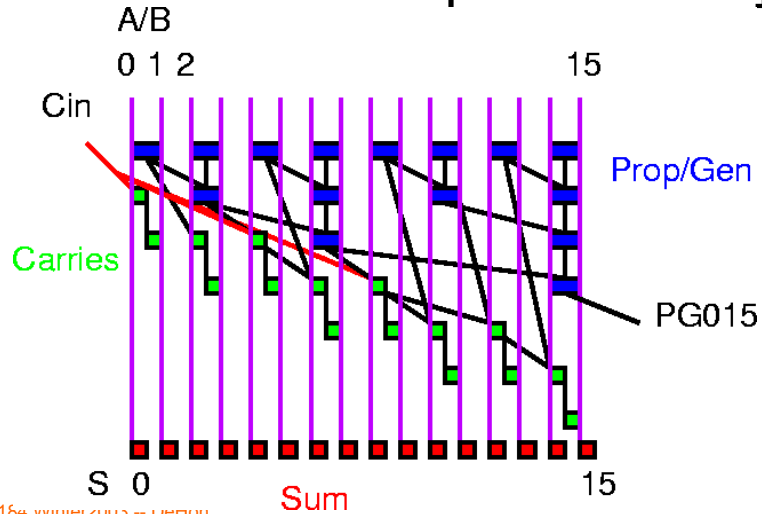
# Resulting RPA [and a few more optimizations]



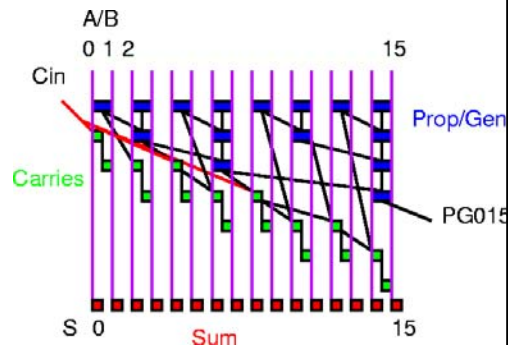
## RPA Analysis

- Delay:  $O(\log(n))$
- Area:  $O(n)$ 
  - maybe  $n \log(n)$  when consider wiring...
- bounded fanout



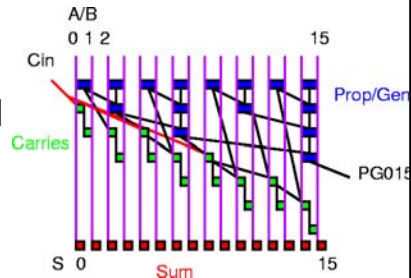
# Constructive RPA

- Each block (I,J) may
  - propagate or squash a carry in
  - generate a carry out
  - can compute  $PG(I,J)$ 
    - in terms of  $PG(I,K)$  and  $PG(K,J)$  ( $I < K < J$ )
- $PG(I,J) + carry(I)$ 
  - is enough to calculate  $carry(J)$



Caltech CS184 Winter2003 -- DeHon

# Resulting RPA

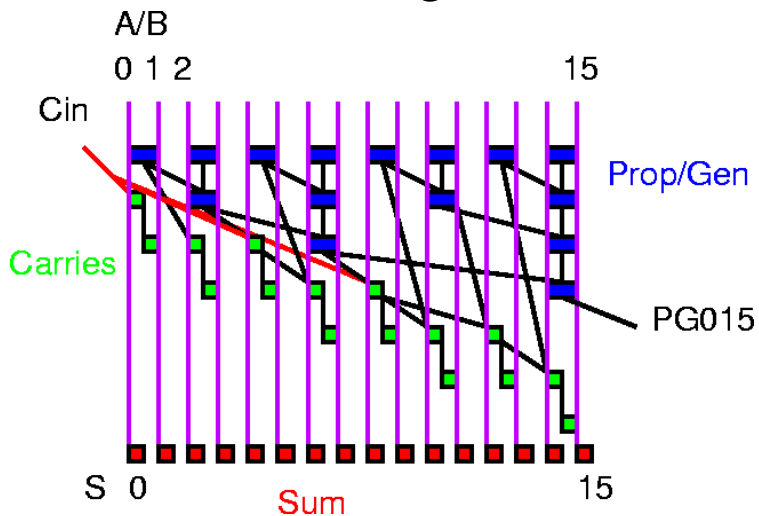

Caltech CS184 Winter2003 -- DeHon

## Note: Constants Matter

- Watch the constants
- Asymptotically this RPA is great
- For small adders can be smaller with
  - fast ripple carry
  - larger combining than 2-ary tree
  - mix of techniques
- ...will depend on the technology primitives and cost functions

Caltech CS184 Winter2003 -- DeHon

## Two's Complement

- Everyone seemed to know Two's complement
- 2's complement:
  - positive numbers in binary
  - negative numbers
    - subtract 1 and invert
    - (or invert and add 1)

Caltech CS184 Winter2003 -- DeHon

## Two's Complement

- $2 = 010$
- $1 = 001$
- $0 = 000$
- $-1 = 111$
- $-2 = 110$

Caltech CS184 Winter2003 -- DeHon

## Addition of Negative Numbers?

- ...just works

A: 111	A: 110	A: 111	A: 111
B: 001	B: 001	B: 010	B: 110
S: 000	S: 111	S: 001	S: 101

Caltech CS184 Winter2003 -- DeHon

# Subtraction

- Negate the subtracted input and use adder
  - which is:
    - invert input and add 1
    - works for both positive and negative input

$$-001 \rightarrow 110 + 1 = 111$$

$$-111 \rightarrow 000 + 1 = 001$$

$$-000 \rightarrow 111 + 1 = 000$$


$$-010 \rightarrow 101 + 1 = 110$$

$$-110 \rightarrow 001 + 1 = 010$$

Caltech CS184 Winter2003 – DeHon
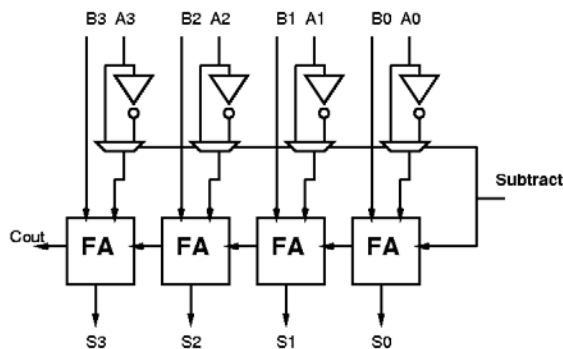
## Subtraction (add/sub)

- **Note:** you can use the “unused” carry input at the LSB to perform the “add 1”



Caltech CS184 Winter2

## Overflow?

A: 111	A: 110	A: 111	A: 111
B: 001	B: 001	B: 010	B: 110
S: 000	S: 111	S: 001	S: 101

A: 001	A: 011	A: 111
B: 001	B: 001	B: 100
S: 010	S: 100	S: 011

- $\text{Overflow} = (\text{A.s} == \text{B.s}) * (\text{A.s} != \text{S.s})$


Caltech CS184 Winter2003 -- DeHon

## Reuse

Caltech CS184 Winter2003 -- DeHon
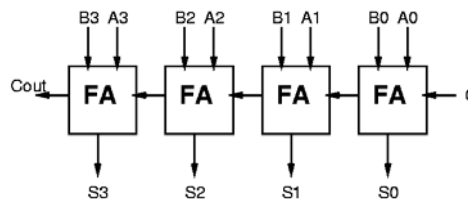
# Reuse


- In general, we want to reuse our components in time
  - not disposable logic
- How do we do that?
  - Wait until done, someone's used output



Caltech CS184 Winter2003 -- I

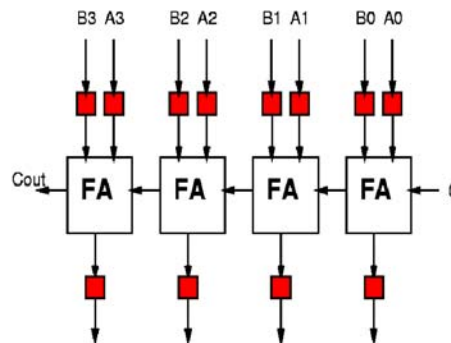
## Reuse: “Waiting” Discipline

- Use registers and timing (or acknowledgements) for orderly progression of data



Caltech CS184 Winter2003 -- DeHon


## Example: 4b Ripple Adder

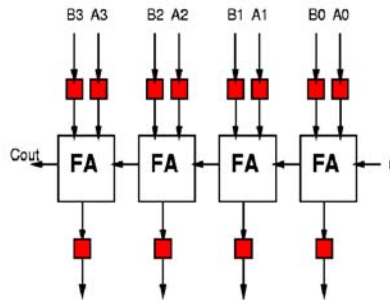

- Recall 2 gates/FA
- Latency: 8 gates to S<sub>3</sub>
- Throughput: 1 result / 8 gate delays max

Caltech CS184 Winter2003 -- DeHon

## Can we do better?

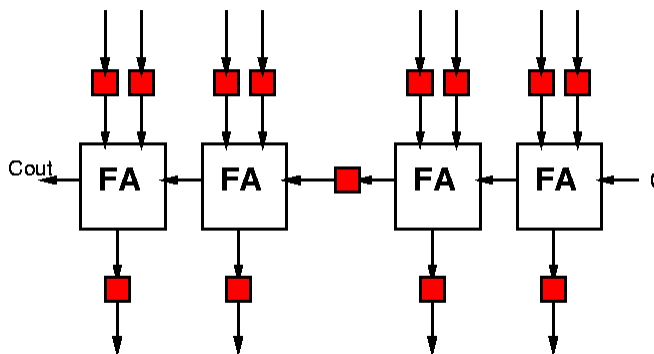


Caltech CS184 Winter2003 -- DeHon


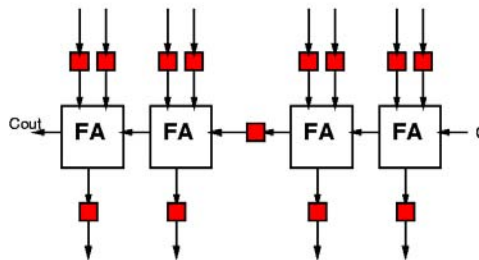
# Stagger Inputs


- Correct if expecting  $A, B[3:2]$  to be staggered one cycle behind  $A, B[1:0]$
- ...and succeeding stage expects  $S[3:2]$  staggered from  $S[1:0]$



Caltech CS184 Winter2003 -- DeHon

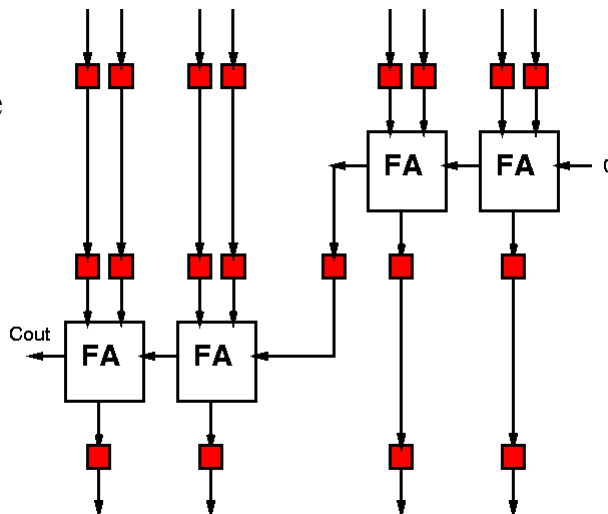
# Align Data / Balance Paths

Good discipline  
to  
line up pipe  
stages  
in diagrams.



Caltech CS184 Winter2003 -- DeHo..

## Example: 4b RA pipe 2

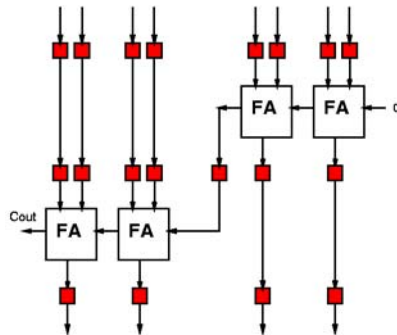

- Recall 2 gates/FA
- Latency: 8 gates to S3
- Throughput: 1 result / 4 gate delays max

Caltech CS184 Winter2003 -- DeHon


## Deeper?

- Can we do it again?
- What's our limit?
- Why would we stop?

Caltech CS184 Winter2003 -- DeHon
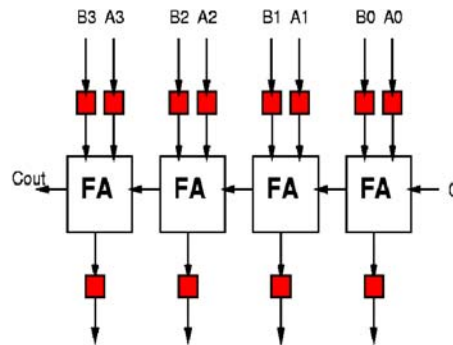
## More Reuse


- Saw could pipeline and reuse FA more frequently
- Suggests we're **wasting** the FA part of the time in non-pipelined



Caltech CS184 Winter2003 -- DeHon
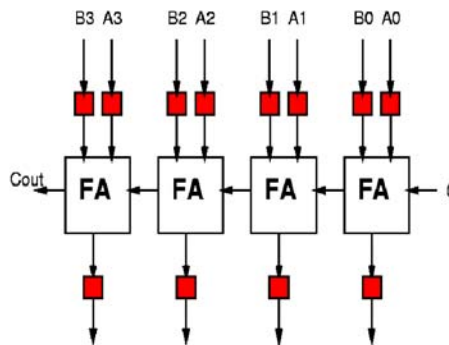
## More Reuse (cont.)


- If we're willing to take 8 gate-delay units, do we need 4 FAs?



Caltech CS184 Winter2003 -- DeHon


# Ripple Add (pipe view)

Can pipeline to FA.

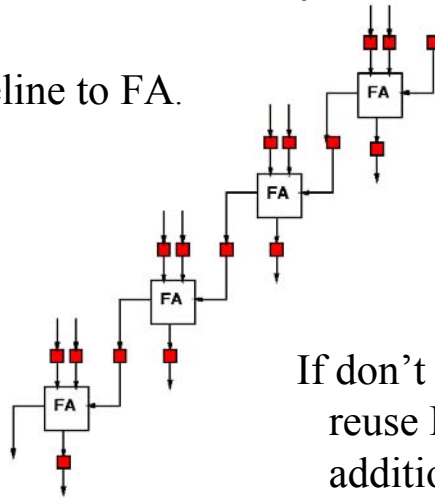

If don't need throughput,  
reuse FA on **SAME**  
addition.


# Bit Serial Addition

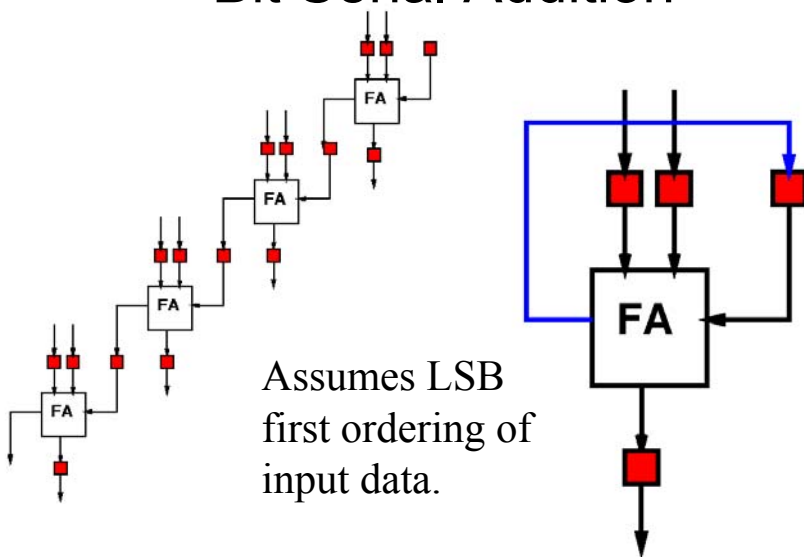

Assumes LSB  
first ordering of  
input data.
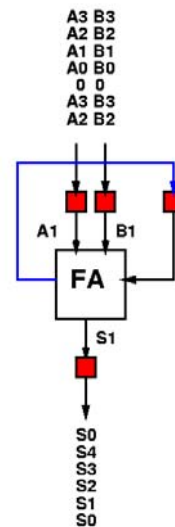
## Bit Serial Addition: Pipelining

- Latency: 8 gate delays
- Throughput: 1 result / 10 gate delays
- Can squash Cout[3] and do in 1 result/8 gate delays
- registers do have time overhead
  - setup, hold time, clock jitter



Caltech CS184 Winter2003 -- DeHon

## Multiplication

- Can be defined in terms of addition
- Ask you to play with implementations and tradeoffs in homework 2

Caltech CS184 Winter2003 -- DeHon

## Compute Function

- Compute:

$$y = Ax^2 + Bx + C$$


- Assume

- $D(\text{Mpy}) > D(\text{Add})$

- $A(\text{Mpy}) > A(\text{Add})$

Caltech CS184 Winter2003 -- DeHon


## Spatial Quadratic

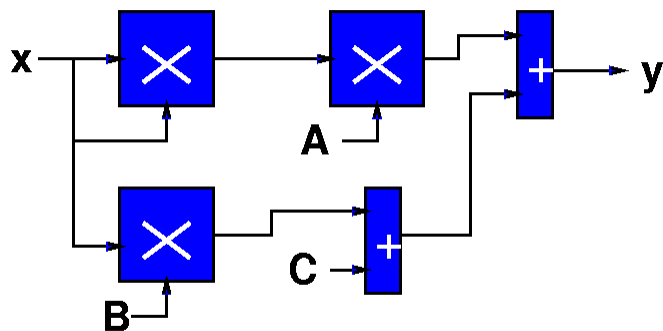

- $D(\text{Quad}) = 2 * D(\text{Mpy}) + D(\text{Add})$
- Throughput  $1 / (2 * D(\text{Mpy}) + D(\text{Add}))$
- $A(\text{Quad}) = 3 * A(\text{Mpy}) + 2 * A(\text{Add})$

Caltech CS184 Winter2003 -- DeHon


## Pipelined Spatial Quadratic

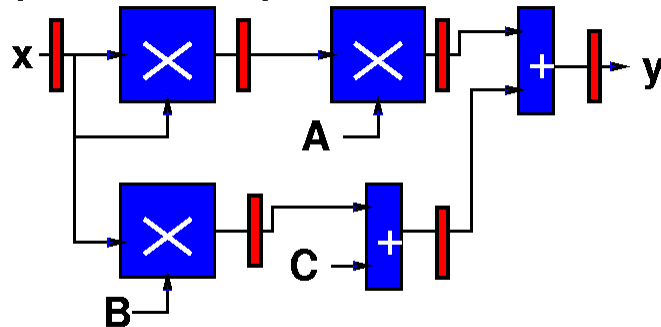

- $D(\text{Quad}) = 3 \cdot D(\text{Mpy})$
- Throughput  $1/D(\text{Mpy})$
- $A(\text{Quad}) = 3 \cdot A(\text{Mpy}) + 2 \cdot A(\text{Add}) + 6A(\text{Reg})$

Caltech CS184 Winter2003 -- DeHon

## Bit Serial Quadratic

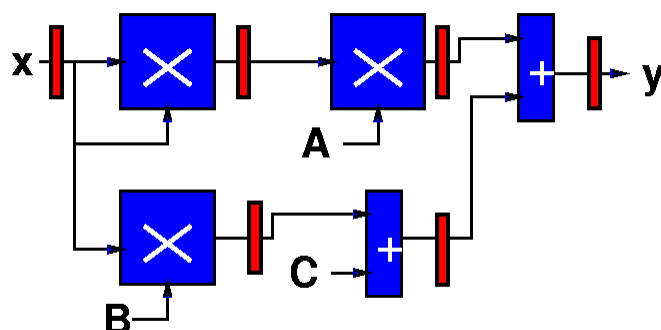

- data width  $w$ ; one bit per cycle
- roughly  $1/w$ -th the area of pipelined spatial
- roughly  $1/w$ -th the throughput
- latency just a little larger than pipelined

Caltech CS184 Winter2003 -- DeHon


## Quadratic with Single Multiplier and Adder?

- We've seen reuse to perform the **same** operation
  - pipelining
  - bit-serial, homogeneous datapath
- We can also reuse a resource in time to perform a different role.
  - Here:  $x*x$ ,  $A*(x*x)$ ,  $B*x$
  - also:  $(Bx)+c$ ,  $(A*x*x)+(Bx+c)$

Caltech CS184 Winter2003 -- DeHon
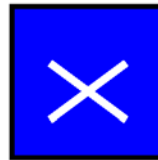
## Quadratic Datapath

- Start with one of each operation
- (alternatives where build multiply from adds...e.g. homework)




Caltech CS184 Winter2003 -- DeHon


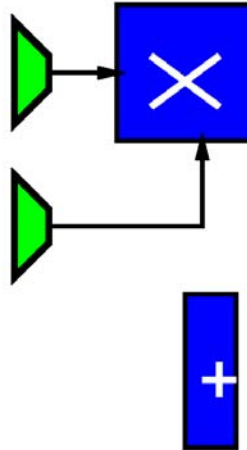
## Quadratic Datapath


- Multiplier servers multiple roles
  - $x^*x$
  - $A^*(x^*x)$
  - $B^*x$
- Will need to be able to steer data (switch interconnections)



Caltech CS184 Winter2003 -- DeHon
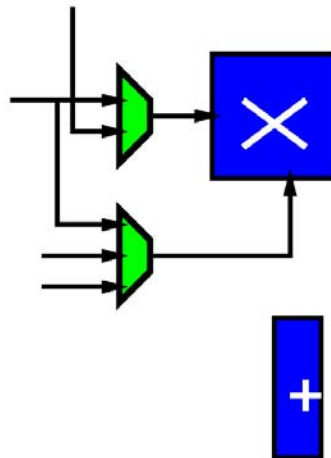
## Quadratic Datapath


- Multiplier servers multiple roles
  - $x^*x$
  - $A^*(x^*x)$
  - $B^*x$
- $x, x^*x$
- $x, A, B$



Caltech CS184 Winter2003 -- DeHon
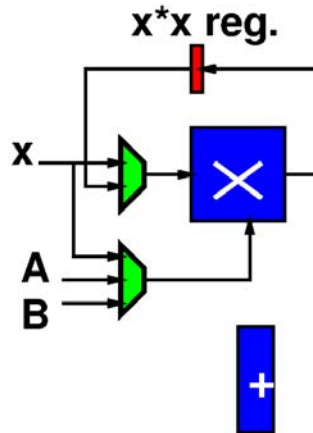
## Quadratic Datapath


- Multiplier servers multiple roles
  - $x^*x$
  - $A^*(x^*x)$
  - $B^*x$
- $x, x^*x$
- $x, A, B$



Caltech CS184 Winter2003 -- DeHon

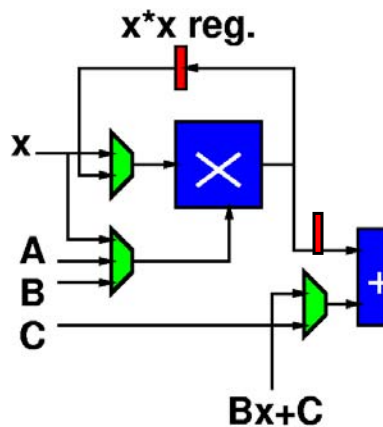
## Quadratic Datapath

- Adder servers multiple roles
  - $(Bx)+c$
  - $(A^*x^*x)+(Bx+c)$
- one always mpy output
- $C, Bx+C$



Caltech CS184 Winter2003 -- DeHon


## Quadratic Datapath

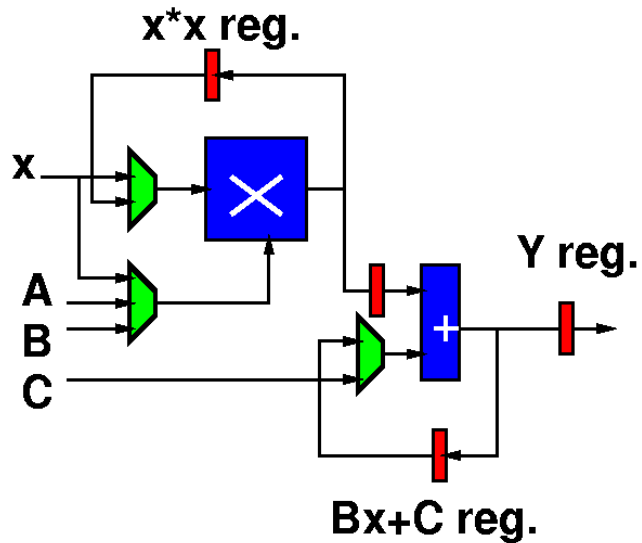

Caltech CS184 Winter

## Quadratic Datapath


- Add input register for  $x$

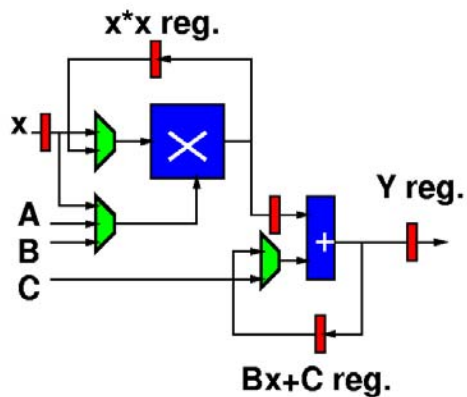

Caltech CS184 Winter2003 -- DeHon
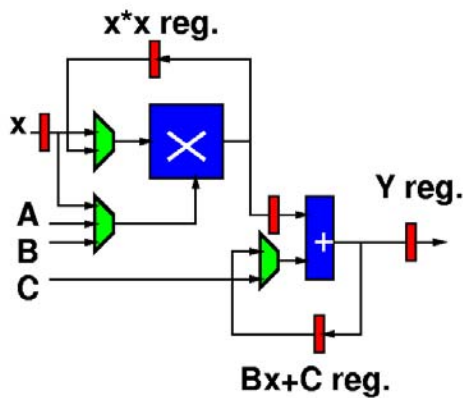
## Quadratic Control

- Now, we just need to control the datapath
- Control:
  - LD x
  - LD  $x^2$
  - MA Select
  - MB Select
  - AB Select
  - LD  $Bx+C$
  - LD Y




Caltech CS184 Winter2003 -- DeHon

## FSMD

- FSMD = FSM + Datapath
- Stylization for building controlled datapaths such as this
- Of course, an FSMD is just an FSM
  - it's often easier to think about as a datapath
  - synthesis, AP&R tools have been notoriously bad about discovering/exploiting datapath structure

Caltech CS184 Winter2003 -- DeHon

# Quadratic FSMD

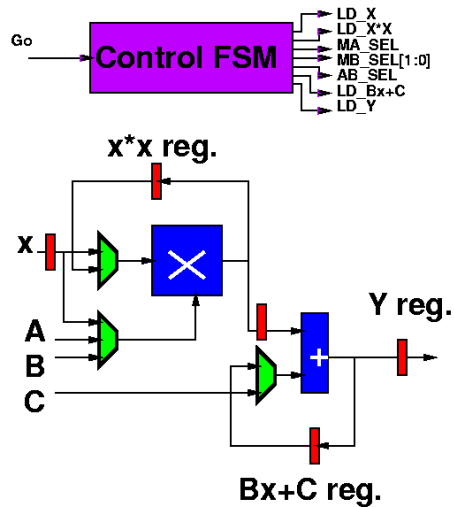

Caltech CS184 Winter2003 -


## Quadratic FSMD Control

- S0: if (go) LD\_X; goto S1  
– else goto S0
- S1: MA\_SEL=x, MB\_SEL[1:0]=x, LD\_x\*x  
– goto S2
- S2: MA\_SEL=x, MB\_SEL[1:0]=B  
– goto S3
- S3: AB\_SEL=C, MA\_SEL=x\*x, MB\_SEL=A  
– goto S4
- S4: AB\_SEL=Bx+C, LD\_Y  
– goto S0

Caltech CS184 Winter2003 -- DeHon
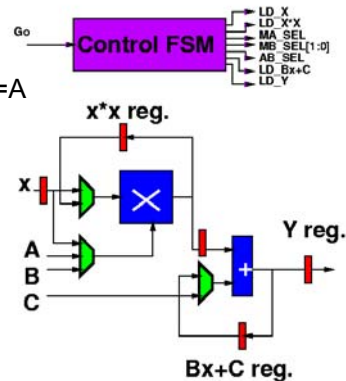
# Quadratic FSMD Control


- S0: if (go) LD\_X; goto S1
  - else goto S0
- S1: MA\_SEL=x,MB\_SEL[1:0]=x, LD\_x\*x
  - goto S2
- S2: MA\_SEL=x,MB\_SEL[1:0]=B
  - goto S3
- S3: AB\_SEL=C,MA\_SEL=x\*x, MB\_SEL=A
  - goto S4
- S4: AB\_SEL=Bx+C, LD\_Y
  - goto S0



Caltech CS184 Winter2003 -- DeHon
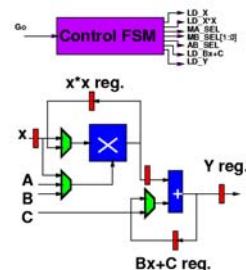
# Quadratic FSM

- Latency:  $5 \cdot (D(\text{MPY}) + D(\text{mux3}))$
- Throughput:  $1/\text{Latency}$
- Area:  $A(\text{Mpy}) + A(\text{Add}) + 5 \cdot A(\text{Reg}) + 2 \cdot A(\text{Mux2}) + A(\text{Mux3}) + A(\text{QFSM})$



Caltech CS184 Winter2003 -- DeHon

# Big Ideas

## [MSB Ideas]

- Can build arithmetic out of logic
- Pipelining:
  - increases parallelism
  - allows reuse in time (same function)
- Control and Sequencing
  - reuse in time for different functions
- Can tradeoff Area and Time

Caltech CS184 Winter2003 -- DeHon

# Big Ideas

## [MSB-1 Ideas]

- Area-Time Tradeoff in Adders
- FSMD control style

Caltech CS184 Winter2003 -- DeHon