

CS184a: Computer Architecture (Structure and Organization)

Day 11: January 31, 2005
Compute 1: LUTs



Caltech CS184 Winter2005 -- DeHon

Previously

- Instruction Space Modeling
 - huge range of densities
 - huge range of efficiencies
 - large architecture space
 - modeling to understand design space
- Empirical Comparisons
 - Ground cost of programmability

2


Today

- Look at Programmable Compute Blocks
- Specifically LUTs Today
- Recurring theme:
 - define parameterized space
 - identify costs and benefits
 - look at typical application requirements
 - compose results, try to find best point

3

Compute Function

 
- What do we use for “compute” function
- Any Universal
 - NAND x
 - ALU
 - LUT



Caltech CS184 Winter2005 -- DeHon


Lookup Table

 - Load bits into table
 - 2^N bits to describe
 - $\rightarrow 2^{2^N}$ different functions
- Table translation
 - performs logic transform



5

Lookup Table

 

6

Caltech CS184 Winter2005 -- DeHon

We could...


- Just build a large memory = large LUT
- Put our function in there
- What's wrong with that?

Caltech CS184 Winter2005 -- DeHon

7

FPGA = Many small LUTs


Alternative to one big LUT

 

8

Caltech CS184 Winter2005 -- DeHon

Toronto FPGA Model

 

9

Caltech CS184 Winter2005 -- DeHon

What's best to use?

- Small LUTs
- Large Memories
- ...small LUTs or large LUTs
- ...or, how big should our memory blocks used to perform computation be?

10

Caltech CS184 Winter2005 -- DeHon


Start to Sort Out: Big vs. Small Luts

- Establish equivalence
 - how many small LUTs equal one big LUT?

Caltech CS184 Winter2005 -- DeHon

11

"gates" in 2-LUT ?

 

12

Caltech CS184 Winter2005 -- DeHon

How Much Logic in a LUT?


- Lower Bound?
 - Concrete: 4-LUTs to implement M-LUT?
 - Not use all inputs?
 - 0 ... maybe 1
 - Use all inputs?
 - $(M-1)/k$ for K-lut
- example M-input AND
 • cover 4 ins w/ first 4-LUT,
 • 3 more and cascade input with each additional

13

Caltech CS184 Winter2005 -- DeHon

How much logic in a LUT?

 - Upper Upper Bound:
 - M-LUT implemented w/ 4-LUTs
 - $M-LUT \leq 2^{M-4} + (2^{M-4}-1) \leq 2^{M-3}$ 4-LUTs



14

Caltech CS184 Winter2005 -- DeHon

How Much?

- Lower Upper Bound:
 - 2^{2^M} functions realizable by M-LUT
 - Say Need n 4-LUTs to cover; compute n :
 - strategy count functions realizable by each
 - $(2^{2^4})^n \geq 2^{2^M}$
 - $n \log(2^{2^4}) \geq \log(2^{2^M})$
 - $n 2^4 \log(2) \geq 2^M \log(2)$
 - $n 2^4 \geq 2^M$
 - $n \geq 2^{M-4}$

15

Caltech CS184 Winter2005 -- DeHon

How Much?

- Combine
 - Lower Upper Bound
 - Upper Lower Bound
 - (number of 4-LUTs in M-LUT)

$$2^{M-4} \leq n \leq 2^{M-3}$$

16

Caltech CS184 Winter2005 -- DeHon

Memories and 4-LUTs

- For the **most complex** functions
 - an M-LUT has $\sim 2^{M-4}$ 4-LUTs
- ◊ SRAM 32Kx8 $\lambda=0.6\mu m$
 - $170M\lambda^2$ (21ns latency)
 - $8 \cdot 2^{11} = 16K$ 4-LUTs
- ◊ XC3042 $\lambda=0.6\mu m$
 - $180M\lambda^2$ (13ns delay per CLB)
 - 288 4-LUTs
- Memory is 50+x denser than FPGA
 - ...and faster

17

Caltech CS184 Winter2005 -- DeHon

Memory and 4-LUTs

- For “regular” functions?
 - ◊ 15-bit parity
 - entire 32Kx8 SRAM
 - 5 4-LUTs
 - (2% of XC3042 $\sim 3.2M\lambda^2 \sim 1/50$ th Memory)
 - ◊ 7b Add
 - entire 32Kx8 SRAM
 - 14 4-LUTs
 - (5% of XC3042, $8.8M\lambda^2 \sim 1/20$ th Memory)

18

Caltech CS184 Winter2005 -- DeHon

LUT + Interconnect

- Interconnect allows us to exploit **structure** in computation
- Already know
 - LUT Area << Interconnect Area
 - Area of an M-LUT on FPGA >> M-LUT Area
- ...but most M-input functions
 - complexity << 2^M



19

Caltech CS184 Winter2005 -- DeHon


Different Instance, Same Concept

- Most general functions are huge
- Applications exhibit **structure**
- Exploit structure to optimize “common” case

20

Caltech CS184 Winter2005 -- DeHon

LUT Count vs. base LUT size

 


Caltech CS184 Winter2005 -- DeHon

21

LUT vs. K

 - DES MCNC Benchmark
 - moderately irregular



22

Caltech CS184 Winter2005 -- DeHon

Toronto Experiments

- Want to determine best K for LUTs
- Bigger LUTs
 - handle complicated functions efficiently
 - less interconnect overhead
- Smaller LUTs
 - handle regular functions efficiently
 - interconnect allows exploitation of compute structure
- What's the typical complexity/structure?

23

Caltech CS184 Winter2005 -- DeHon

Familiar Systematization


- Define a design/optimization space
 - pick key parameters
 - e.g. K = number of LUT inputs
- Build a cost model
- Map designs
- Look at resource costs at each point
- Compose:
 - Logical Resources \oplus Resource Cost
- Look for best design points

24

Caltech CS184 Winter2005 -- DeHon

Toronto LUT Size

 
- Map to K-LUT
 - use Chortle
- Route to determine wiring tracks
 - global route
 - different channel width W for each benchmark
- Area Model for K and W
 - A_{lut} exponential in K
 - Interconnect area based on switch count.



25

Caltech CS184 Winter2005 -- DeHon

LUT Area vs. K

 


- Routing Area roughly linear in K ?

26

Caltech CS184 Winter2005 -- DeHon

Mapped LUT Area


- Compose Mapped LUTs and Area Model

 

27

Caltech CS184 Winter2005 -- DeHon

Mapped Area vs. LUT K

 

28

N.B. unusual case minimum area at K=3

Caltech CS184 Winter2005 -- DeHon


Toronto Result

- Minimum LUT Area
 - at $K=4$
 - Important to note minimum on previous slides based on particular cost model
 - robust for different switch sizes
 - (wire widths)
 - [see graphs in paper]

29

Caltech CS184 Winter2005 -- DeHon

Implications

 


30

Caltech CS184 Winter2005 -- DeHon

Implications

 - Custom? / Gate Arrays?
- More restricted logic functions?



Relate to Sequential?

- How does this result relate to sequential execution case?
- Number of LUTs = Number of Cycles
- Interconnect Cost?
 - Naïve
 - structure in practice?
- Instruction Cost?

32

Delay

Back to Spatial


Caltech CS184 Winter2005 -- DeHon

33

Delay?

- Circuit Depth in LUTs?


- “Simple Function” → M-input AND

 

34

Delay?

 - M-input “Complex” function
 - 1 table lookup for M-LUT
 - Lower bound: $\lceil \log_k(2^{(M-k)}) \rceil + 1$
 - $\log_k(2^{(M-k)}) = (M-k)\log_k(2)$



35

Some Math


- $Y = \log_k(2)$
- $k^Y = 2$
- $Y \log_2(k) = 1$
- $Y = 1/\log_2(k)$
- $\log_k(2) = 1/\log_2(k)$
- $(M-k)\log_k(2)$
- $(M-k)/\log_2(k)$

Caltech CS184 Winter2005 -- DeHon

36


Delay?

 - M-input “Complex” function
 - Lower bound: $\lceil \log_k(2^{(M-k)}) \rceil + 1$
 - $-\log_k(2^{(M-k)}) = (M-k)\log_k(2)$
 - Lower Bound: $\lceil (M-k)/\log_2(k) \rceil + 1$




Delay?

 - M-input “Complex” function
 - Upper Bound:
 - use each k-lut as a $k \cdot \log_2(k)$ input mux
 - Upper Bound: $\lceil (M-k)/\log_2(k \cdot \log_2(k)) \rceil + 1$



Delay?

 - M-input “Complex” function
 - 1 table lookup for M-LUT
 - between: $\lceil (M-k)/\log_2(k) \rceil + 1$
 - and $\lceil (M-k)/\log_2(k \cdot \log_2(k)) \rceil + 1$




Delay

- Simple:** $\log M$
- Complex:** linear in M
- Both scale as $1/\log(k)$

Caltech CS184 Winter2005 -- DeHon

40


Circuit Depth vs. K

 

LUT Delay vs. K


- For small LUTs:
 
$$-t_{LUT} \approx c_0 + c_1 \times K$$
- Large LUTs:
 - add length term
 - $c_2 \times \sqrt{2^K}$
- Plus Wire Delay
 - $\sim \sqrt{\text{area}}$



42

Delay vs. K

 

Why not satisfied with this model?

Caltech CS184 Winter2005 -- DeHon

43

Observation

- General interconnect is expensive
- “Larger” logic blocks
 - less interconnect crossing
 - lower interconnect delay
 - get larger
 - get slower
 - Happens faster than modeled here due to area
 - less area efficient
 - don’t match structure in computation

Caltech CS184 Winter2005 -- DeHon

44

Big Ideas [MSB Ideas]

- Memory most dense programmable structure for the **most complex** functions
- Memory inefficient (scales poorly) for structured compute tasks
- Most tasks have some structure
- Programmable interconnect allows us to exploit that structure

Caltech CS184 Winter2005 -- DeHon

45

Big Ideas [MSB-1 Ideas]

- Area
 - LUT count decrease w/ K, but slower than exponential
 - LUT size increase w/ K
 - exponential LUT function
 - empirically linear routing area
 - Minimum area around K=4

Caltech CS184 Winter2005 -- DeHon

46

Big Ideas [MSB-1 Ideas]

- Delay
 - LUT depth decreases with K
 - in practice closer to $\log(K)$
 - Delay increases with K
 - small K linear + large fixed term
 - minimum around 5-6

Caltech CS184 Winter2005 -- DeHon

47