

# CS184a: Computer Architecture (Structure and Organization)

Day 3: January 10, 2005  
Arithmetic and Pipelining



Caltech CS184 Winter2005 -- DeHon

## Last Time

- Boolean logic  $\Rightarrow$  computing **any** finite function
- Sequential logic  $\Rightarrow$  computing **any** finite automata
  - included some functions of unbounded size
- Saw gates and registers
  - ...and a few properties of logic

Caltech CS184 Winter2005 -- DeHon

## Today

- Addition
  - organization
  - design space
  - area, time
- Pipelining
- Temporal Reuse
  - area-time tradeoffs

Caltech CS184 Winter2005 -- DeHon

## Example: Bit Level Addition

- Addition
    - (everyone knows how to do addition base 2, right?)
- C: 1101101000**  
**A: 01101101010**  
**B: 01100101100**  
**S: 11110010110**

Caltech CS184 Winter2005 -- DeHon

## Addition Base 2

- $A = a_{n-1} * 2^{(n-1)} + a_{n-2} * 2^{(n-2)} + \dots + a_1 * 2^1 + a_0 * 2^0$   
 $= \sum (a_i * 2^i)$
- $S = A + B$
- $s_i = (\text{xor } \text{carry}_i \text{ } (\text{xor } a_i \text{ } b_i))$
- $\text{carry}_i = (a_{i-1} + b_{i-1} + \text{carry}_{i-1}) \geq 2$   
 $= (\text{or } (\text{and } a_{i-1} \text{ } b_{i-1}) \text{ } (\text{and } a_{i-1} \text{ } \text{carry}_{i-1}) \text{ } (\text{and } b_{i-1} \text{ } \text{carry}_{i-1}))$

Caltech CS184 Winter2005 -- DeHon


## Adder Bit

- $S = (\text{xor } a \text{ } b \text{ } \text{carry})$
- $t = (\text{xor } 2 \text{ } a \text{ } b)$ ;  $s = (\text{xor } 2 \text{ } t \text{ } \text{carry})$
- $\text{xor } 2 = (\text{and } (\text{not } (\text{and } 2 \text{ } a \text{ } b)) \text{ } (\text{not } (\text{and } 2 \text{ } (\text{not } a) \text{ } (\text{not } b))))$
- $\text{carry} = (\text{not } (\text{and } 2 \text{ } (\text{not } (\text{and } 2 \text{ } a \text{ } b)) \text{ } (\text{and } 2 \text{ } (\text{not } (\text{and } 2 \text{ } b \text{ } \text{carry})) \text{ } (\text{not } (\text{and } 2 \text{ } a \text{ } \text{carry}))))))$

Caltech CS184 Winter2005 -- DeHon

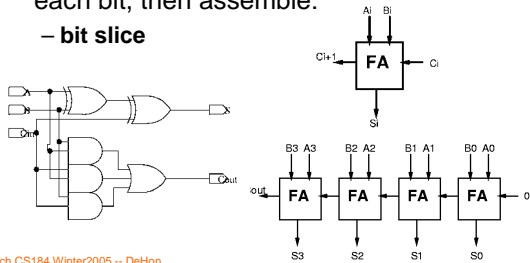
## Ripple Carry Addition

- Shown operation of each bit
- Often convenient to define logic for each bit, then assemble:
  - bit slice



Caltech CS184 Winter2005 -- DeHon

## Ripple Carry Analysis

 

- Area: O(N) [6n]
- Delay: O(N) [2n]

Caltech CS184 Winter2005 -- DeHon

## Can we do better?

Caltech CS184 Winter2005 -- DeHon


## Important Observation

- Do we have to wait for the carry to show up to begin doing useful work?
  - We do have to know the carry to get the right answer.
  - But, it can only take on two values

Caltech CS184 Winter2005 -- DeHon
 
## Idea

- Compute both possible values and select correct result when we know the answer



Caltech CS184 Winter2005 -- D

## Preliminary Analysis

- DRA--Delay Ripple Adder
- $DRA(n) = k \cdot n$
- $DRA(n) = 2 \cdot DRA(n/2)$
- DP2A-- Delay Predictive Adder
- $DP2A = DRA(n/2) + D(\text{mux}2)$
- ...almost half the delay!


Caltech CS184 Winter2005 -- DeHon

## Recurse

- If something works once, do it again.
- Use the predictive adder to implement the first half of the addition

Caltech CS184 Winter2005 -- DeHon

## Recurse

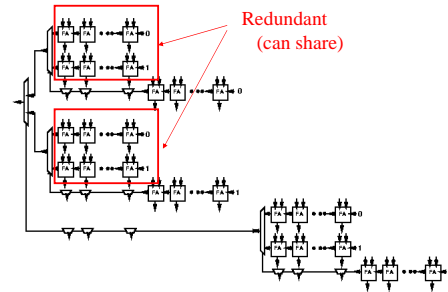

Caltech CS184 Winter2005 -- DeHon

## Recurse

- If something works once, do it again.
- Use the predictive adder to implement the first half of the addition
- $DP4A(n) = DRA(n/4) + D(\text{mux}2) + D(\text{mux}2)$
- $DP4A(n) = DRA(n/4) + 2 * D(\text{mux}2)$

Caltech CS184 Winter2005 -- DeHon

## Recurse

- By now we realize we've been using the wrong recursion
  - should be using the DPA in the recursion
- $DPA(n) = DPA(n/2) + D(\text{mux}2)$
- $DPA(n) = \log_2(n) * D(\text{mux}2) + C$

Caltech CS184 Winter2005 -- DeHon


## Another Way

(Parallel Prefix)

Caltech CS184 Winter2005 -- DeHon
 
## CLA


- Think about each adder bit as a computing a function on the carry in
  - $C[i] = g(c[i-1])$
  - Particular function  $f$  will depend on  $a[i]$ ,  $b[i]$
  - $G = f(a, b)$



Caltech CS184 Winter2005 -- DeHon
 
## Functions

- What functions can  $g(c[i-1])$  be?
  - $g(x)=1$ 
    - $a[i]=b[i]=1$
  - $g(x)=x$ 
    - $a[i] \text{ xor } b[i]=1$
  - $g(x)=0$ 
    - $A[i]=b[i]=0$



Caltech CS184 Winter2005 -- DeHon


## Functions

- What functions can  $g(c[i-1])$  be?
  - $g(x)=1$  Generate
    - $a[i]=b[i]=1$
  - $g(x)=x$  Propagate
    - $a[i] \text{ xor } b[i]=1$
  - $g(x)=0$  Squash
    - $A[i]=b[i]=0$

Caltech CS184 Winter2005 -- DeHon
 
## Combining

- Want to combine functions
  - Compute  $c[i]=g(g_{i-1}(c[i-2]))$
  - Compute compose of two functions
- What functions will the compose of two of these functions be?
  - Same as before
    - Propagate, generate, squash



Caltech CS184 Winter2005 -- DeHon

## Compose Rules (LSB MSB)

- GG
- GP
- GS
- PG
- PP
- PS
- SG
- SP
- SS

Caltech CS184 Winter2005 -- DeHon


## Compose Rules (LSB MSB)

- GG = G
- GP = G
- GS = S
- PG = G
- PP = P
- PS = S
- SG = G
- SP = S
- SS = S



Caltech CS184 Winter2005 -- DeHon
 
## Combining

- Do it again...
- Combine  $g[i-3, i-2]$  and  $g[i-1, i]$
- What do we get?



Caltech CS184 Winter2005 -- DeHon

 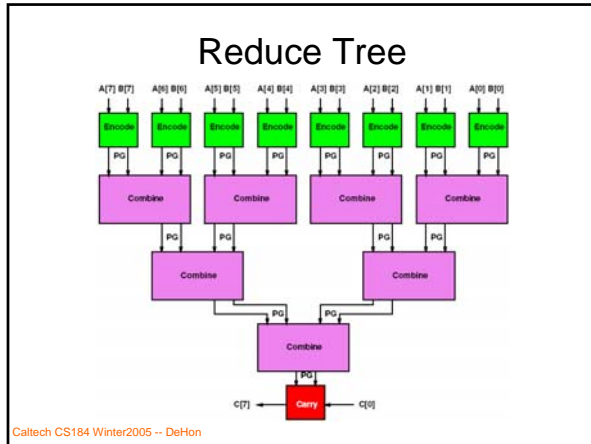

- ### Parallel Prefix
- Important **Pattern**
  - Applicable any time operation is associative
  - Function Composition is always associative
- Caltech CS184 Winter2005 -- DeHon

- ### Note: Constants Matter
- Watch the constants
  - Asymptotically this RPA is great
  - For small adders can be smaller with
    - fast ripple carry
    - larger combining than 2-ary tree
    - mix of techniques
  - ...will depend on the technology primitives and cost functions
- Caltech CS184 Winter2005 -- DeHon

- ### Two's Complement
- Everyone seemed to know Two's complement
  - 2's complement:
    - positive numbers in binary
    - negative numbers
      - subtract 1 and invert
      - (or invert and add 1)
- Caltech CS184 Winter2005 -- DeHon

- ### Two's Complement
- $2 = 010$
  - $1 = 001$
  - $0 = 000$
  - $-1 = 111$
  - $-2 = 110$
- Caltech CS184 Winter2005 -- DeHon

## Addition of Negative Numbers?

- ...just works

A: 111	A: 110	A: 111	A: 111
B: 001	B: 001	B: 010	B: 110
S: 000	S: 111	S: 001	S: 101

Caltech CS184 Winter2005 -- DeHon

## Subtraction

- Negate the subtracted input and use adder – which is:

- invert input and add 1
- works for both positive and negative input

$$-001 \rightarrow 110 + 1 = 111$$

$$-111 \rightarrow 000 + 1 = 001$$

$$-000 \rightarrow 111 + 1 = 000$$


$$-010 \rightarrow 101 + 1 = 110$$

$$-110 \rightarrow 001 + 1 = 010$$

Caltech CS184 Winter2005 -- DeHon
 
## Subtraction (add/sub)

- **Note:** you can use the “unused” carry input at the LSB to perform the “add 1”



Caltech CS184 Winter2005 -- DeHon

## Overflow?

A: 111	A: 110	A: 111	A: 111
B: 001	B: 001	B: 010	B: 110
S: 000	S: 111	S: 001	S: 101

A: 001	A: 011	A: 111
B: 001	B: 001	B: 100
S: 010	S: 100	S: 011

- Overflow =  $(A.s == B.s) * (A.s != S.s)$


Caltech CS184 Winter2005 -- DeHon

## Reuse

Caltech CS184 Winter2005 -- DeHon
 
## Reuse


- In general, we want to reuse our components in time – not disposable logic
- How do we do that? – Wait until done, someone’s used output



Caltech CS184 Winter2005 -- DeHon

 
## Reuse: "Waiting" Discipline

- Use registers and timing (or acknowledgements) for orderly progression of data



Caltech CS184 Winter2005 -- DeHon


## Example: 4b Ripple Adder

 

- Recall 2 gates/FA
- Latency: 8 gates to S3
- Throughput: 1 result / 8 gate delays max

Caltech CS184 Winter2005 -- DeHon


## Can we do better?

 

Caltech CS184 Winter2005 -- DeHon
 
## Stagger Inputs


- Correct if expecting A,B[3:2] to be staggered one cycle behind A,B[1:0]
- ...and succeeding stage expects S[3:2] staggered from S[1:0]



Caltech CS184 Winter2005 -- DeHon

 
## Align Data / Balance Paths

Good discipline to line up pipe stages in diagrams.



Caltech CS184 Winter2005 -- DeHon

## Example: 4b RA pipe 2

 

- Recall 2 gates/FA
- Latency: 8 gates to S3
- Throughput: 1 result / 4 gate delays max

Caltech CS184 Winter2005 -- DeHon


## Deeper?

- Can we do it again?
- What's our limit?
- Why would we stop?

Caltech CS184 Winter2005 -- DeHon
 
## More Reuse


- Saw could pipeline and reuse FA more frequently
- Suggests we're **wasting** the FA part of the time in non-pipelined



Caltech CS184 Winter2005 -- DeHon
 
## More Reuse (cont.)


- If we're willing to take 8 gate-delay units, do we need 4 FAs?



Caltech CS184 Winter2005 -- DeHon

## Ripple Add (pipe view)


Can pipeline to FA.

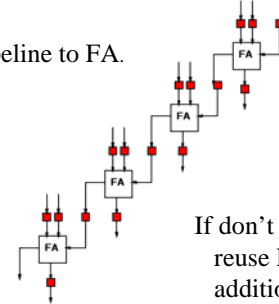

If don't need throughput, reuse FA on **SAME** addition.

Caltech CS184 Winter2005 -- DeHon

## Bit Serial Addition

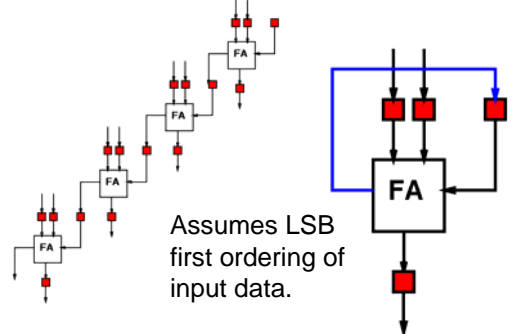


Assumes LSB first ordering of input data.

Caltech CS184 Winter2005 -- DeHon
 
## Bit Serial Addition: Pipelining

- Latency: 8 gate delays
- Throughput: 1 result / 10 gate delays
- Can squash  $Cout[3]$  and do in 1 result/8 gate delays
- registers do have time overhead
  - setup, hold time, clock jitter



Caltech CS184 Winter2005 -- DeHon



## Multiplication

- Can be defined in terms of addition
- Ask you to play with implementations and tradeoffs in homework 2


Caltech CS184 Winter2005 -- DeHon

## Compute Function

- Compute:  
 $y = Ax^2 + Bx + C$
- Assume
  - $D(\text{Mpy}) > D(\text{Add})$
  - $A(\text{Mpy}) > A(\text{Add})$

Caltech CS184 Winter2005 -- DeHon


## Spatial Quadratic

 

- $D(\text{Quad}) = 2 * D(\text{Mpy}) + D(\text{Add})$
- Throughput  $1 / (2 * D(\text{Mpy}) + D(\text{Add}))$
- $A(\text{Quad}) = 3 * A(\text{Mpy}) + 2 * A(\text{Add})$

Caltech CS184 Winter2005 -- DeHon


## Pipelined Spatial Quadratic

 

- $D(\text{Quad}) = 3 * D(\text{Mpy})$
- Throughput  $1 / D(\text{Mpy})$
- $A(\text{Quad}) = 3 * A(\text{Mpy}) + 2 * A(\text{Add}) + 6A(\text{Reg})$

Caltech CS184 Winter2005 -- DeHon

## Bit Serial Quadratic

 

- data width  $w$ ; one bit per cycle
- roughly  $1/w$ -th the area of pipelined spatial
- roughly  $1/w$ -th the throughput
- latency just a little larger than pipelined

Caltech CS184 Winter2005 -- DeHon


## Quadratic with Single Multiplier and Adder?

- We've seen reuse to perform the **same** operation
  - pipelining
  - bit-serial, homogeneous datapath
- We can also reuse a resource in time to perform a different role.
  - Here:  $x * x$ ,  $A * (x * x)$ ,  $B * x$
  - also:  $(Bx) + c$ ,  $(A * x * x) + (Bx + c)$

Caltech CS184 Winter2005 -- DeHon
 
## Quadratic Datapath


- Start with one of each operation
- (alternatives where build multiply from adds...e.g. homework)



Caltech CS184 Winter2005 -- DeHon
 
## Quadratic Datapath


- Multiplier servers multiple roles
  - $x^2x$
  - $A^*(x^2x)$
  - $B^*x$
- Will need to be able to steer data (switch interconnections)



Caltech CS184 Winter2005 -- DeHon
 
## Quadratic Datapath


- Multiplier servers multiple roles
  - $x^2x$
  - $A^*(x^2x)$
  - $B^*x$
- $x, x^2x$
- $x, A, B$



Caltech CS184 Winter2005 -- DeHon
 
## Quadratic Datapath


- Multiplier servers multiple roles
  - $x^2x$
  - $A^*(x^2x)$
  - $B^*x$
- $x, x^2x$
- $x, A, B$



Caltech CS184 Winter2005 -- DeHon

 
## Quadratic Datapath

- Adder servers multiple roles
  - $(Bx)+c$
  - $(A^*x^2x)+(Bx+c)$
- one always mpy output
- $C, Bx+C$



Caltech CS184 Winter2005 -- DeHon


## Quadratic Datapath

 

Caltech CS184 Winter

## Quadratic Datapath


- Add input register for x

 

Caltech CS184 Winter2005 -- DeHon
 
## Quadratic Control

- Now, we just need to control the datapath
- Control:
  - LD x
  - LD  $x^2$
  - MA Select
  - MB Select
  - AB Select
  - LD  $Bx+C$
  - LD Y




Caltech CS184 Winter2005 -- DeHon

## FSMD

- FSMD = FSM + Datapath
- Stylization for building controlled datapaths such as this (a **pattern**)
- Of course, an FSMD is just an FSM
  - it's often easier to think about as a datapath
  - synthesis, AP&R tools have been notoriously bad about discovering/exploiting datapath structure

Caltech CS184 Winter2005 -- DeHon

## Quadratic FSMD

 

Caltech CS184 Winter2005 --


## Quadratic FSMD Control

- S0: if (go) LD\_X; goto S1
  - else goto S0
- S1: MA\_SEL=x, MB\_SEL[1:0]=x, LD\_x<sup>2</sup>
  - goto S2
- S2: MA\_SEL=x, MB\_SEL[1:0]=B
  - goto S3
- S3: AB\_SEL=C, MA\_SEL=x<sup>2</sup>, MB\_SEL=A
  - goto S4
- S4: AB\_SEL=Bx+C, LD\_Y
  - goto S0

Caltech CS184 Winter2005 -- DeHon
 
## Quadratic FSMD Control


- S0: if (go) LD\_X; goto S1
  - else goto S0
- S1: MA\_SEL=x, MB\_SEL[1:0]=x, LD\_x<sup>2</sup>
  - goto S2
- S2: MA\_SEL=x, MB\_SEL[1:0]=B
  - goto S3
- S3: AB\_SEL=C, MA\_SEL=x<sup>2</sup>, MB\_SEL=A
  - goto S4
- S4: AB\_SEL=Bx+C, LD\_Y
  - goto S0



Caltech CS184 Winter2005 -- DeHon
 
## Quadratic FSM

- Latency:  $5 \cdot (D(\text{MPY}) + D(\text{mux3}))$
- Throughput:  $1/\text{Latency}$
- Area:  $A(\text{Mpy}) + A(\text{Add}) + 5 \cdot A(\text{Reg}) + 2 \cdot A(\text{Mux2}) + A(\text{Mux3}) + A(\text{QFSM})$



Caltech CS184 Winter2005 -- DeHon

## Big Ideas [MSB Ideas]

- Can build arithmetic out of logic
- Pipelining:
  - increases parallelism
  - allows reuse in time (same function)
- Control and Sequencing
  - reuse in time for different functions
- Can tradeoff Area and Time

Caltech CS184 Winter2005 -- DeHon

## Big Ideas [MSB-1 Ideas]

- Area-Time Tradeoff in Adders
- Parallel Prefix
- FSM control style

Caltech CS184 Winter2005 -- DeHon